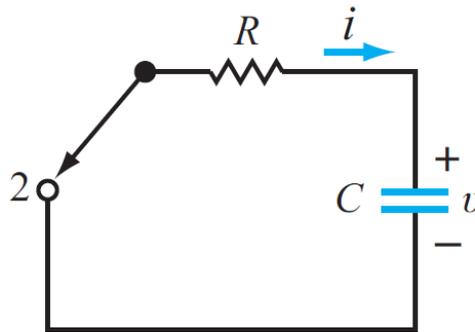


Natural Response of an RC Circuit

Consider the circuit below. Assume we know that the capacitor, C , has an initial voltage $v(0)$ across it. What is the voltage, v , across C , for $t \geq 0$?



Applying KVL, we can write:

$$Ri + v = 0$$

Substituting the i-v relation for a capacitor, we obtain:

$$RC \frac{dv}{dt} + v = 0$$

We can clean this up a bit by dividing by RC :

$$\frac{dv}{dt} + av = 0$$

Where:

$$a = \frac{1}{RC}$$

This is a differential equation. It turns out the solution to the differential equation in the blue box above is:

$$v(t) = v(0) e^{-t/\tau}$$


where:

$$\tau = RC \quad (\text{s})$$

Once we know the voltage, v , we can also determine:

- the current, i (since $i = C \cdot dv/dt$ for a capacitor)
- the power being absorbed or injected by the capacitor (since $P = i \cdot v$)
- the energy stored in the capacitor at any time (since $U = \int P$ or $\frac{1}{2} \cdot C v^2$)

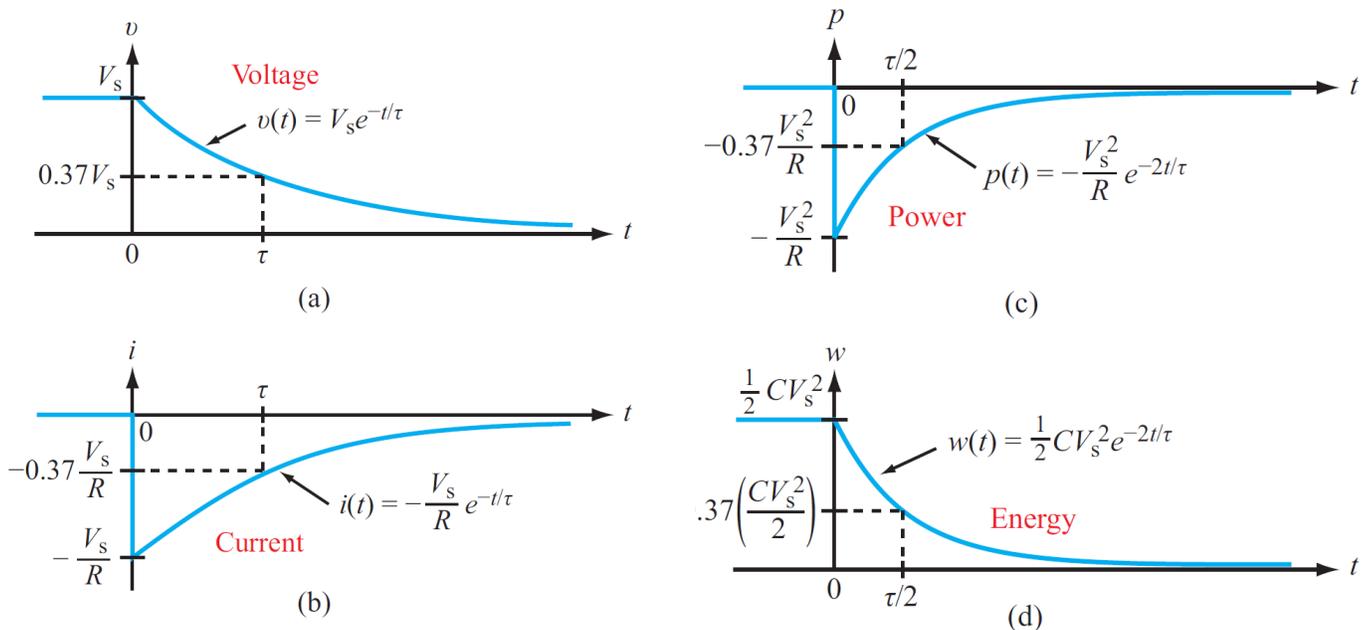All four variables are plotted below for this circuit.



What does the *time constant, τ* , tell us?

The magnitude of the time constant τ is a measure of how fast or how slowly a circuit responds to a sudden change.

- Notice that the units of τ are seconds (that is ohms * farads = seconds).
- Notice in figure (a) above, that after 1τ , the capacitor has discharged to 0.37 of the initial value.
- After about 5τ , $v(t)$ has dropped to $<1\%$ of its original value. Engineers assume 5τ is long enough for particular RC circuit to charge or discharge to its final value.