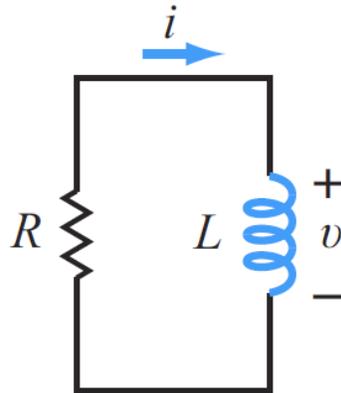


## Natural Response of an RL Circuit

Consider the circuit below. Assume we know that the inductor,  $L$ , has an initial current  $i(0)$  through it. What is the current,  $i$ , through  $L$ , for  $t \geq 0$ ?



Applying KVL, we can write:

$$Ri + L \frac{di}{dt} = 0$$

We can clean this up a bit by dividing by  $L$ :

$$\frac{di}{dt} + ai = 0$$

Where:

$$a = \frac{R}{L}$$

This is a differential equation. Just as in the RC case, it turns out the solution to the differential equation in the blue box above is:

$$i(t) = i(0) e^{-t/\tau} \quad (\text{for } t \geq 0),$$

where:

$$\tau = \frac{1}{a} = \frac{L}{R}.$$

Once we know the current,  $i$ , we can also determine:

- the voltage across the inductor,  $v$  (since  $v = L \cdot di/dt$  for an inductor)
- the power being absorbed or injected by the inductor (since  $P = i \cdot v$ )
- the energy stored in the inductor at any time (since  $U = \int P$  or  $\frac{1}{2} \cdot Li^2$ )

### What does the *time constant*, $\tau$ , tell us?

Just as with the RC circuit, the magnitude of the time constant  $\tau$  is a measure of how fast or how slowly a circuit responds to a sudden change.

- Notice that the units of  $\tau$  are seconds (that is henrys / ohms = seconds).
- After  $1 \tau$ , the inductor has discharged to 0.37 of the initial value.
- After about  $5\tau$ ,  $v(t)$  has dropped to <1% of its original value. Engineers assume  $5\tau$  is long enough for particular RL circuit to charge or discharge to its final value.