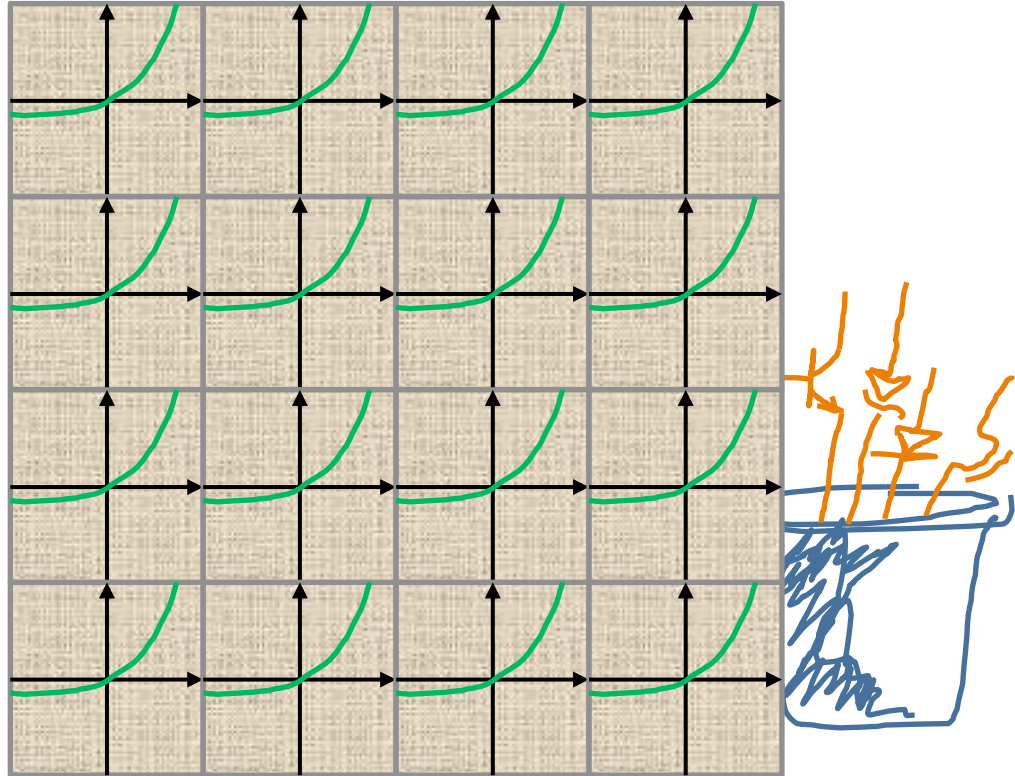


Nonlinear Circuits

$$i = a \cdot v^2$$

Reading Chap 4.1 - 4.3



Review

■ Discretize matter $\rightarrow$ Lumped circuit abstraction $\leftarrow$

m1 $\blacktriangleright$ KVL, KCL, $i-v$ $\leftarrow$

m2 $\blacktriangleright$ Composition rules

$\rightarrow$ m3 $\blacktriangleright$ Node method

m4 $\blacktriangleright$ Superposition

m5 $\blacktriangleright$ Thévenin, Norton

any circuit

linear circuits


*linear subjects
as well*




Review

■ Discretize value $\rightarrow$ Digital abstraction $\leftarrow$

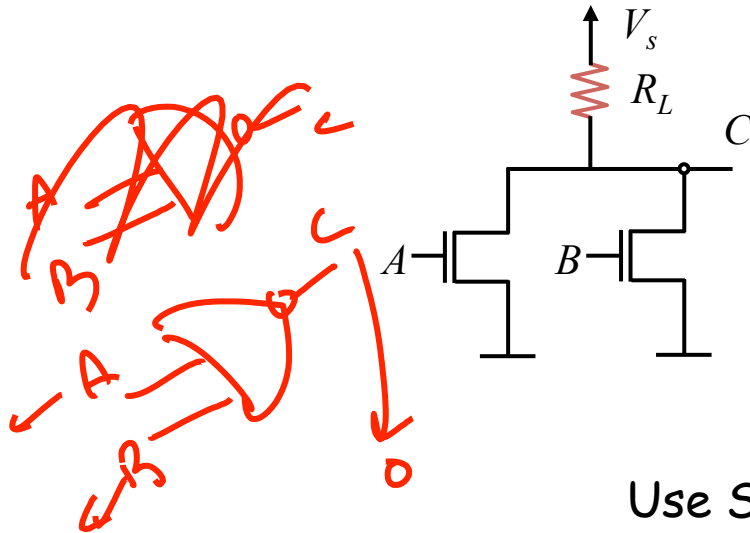
► Subcircuits for given “switch” setting are linear! So, all 5 methods (m1 - m5) can be applied



$A=1$
 $B=1$

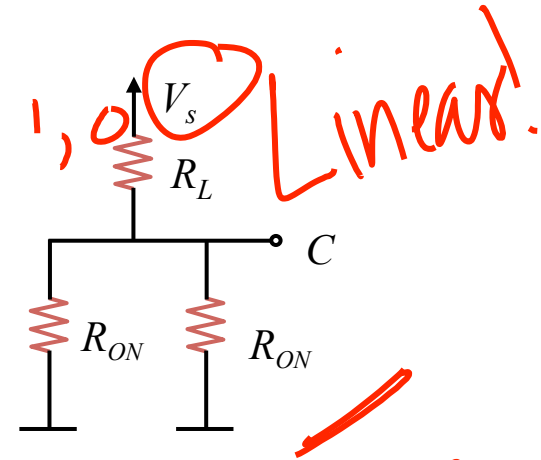

$A=1$
 $B=0$

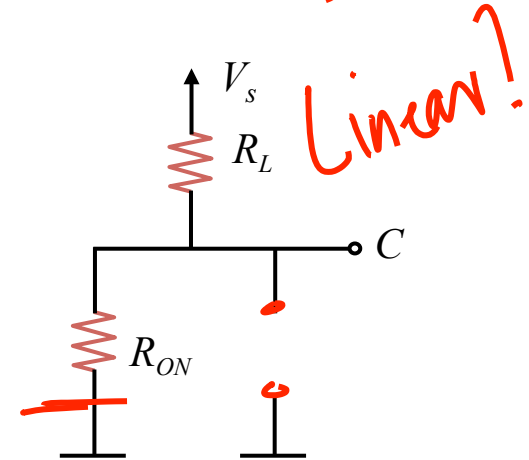

Use SR MOSFET Model



Today

■ Nonlinear circuits and their analysis

- ▶ Analytical method based on m1, m2, m3 ← *of circuit analysis*
- ▶ Graphical method *~~m4, m5~~*
- ▶ Piecewise linear method — *not a focus area for 6.002x*
- ▶ Introduction to incremental analysis *or small signal method*

Non-Linear Elements



A square law two-terminal element

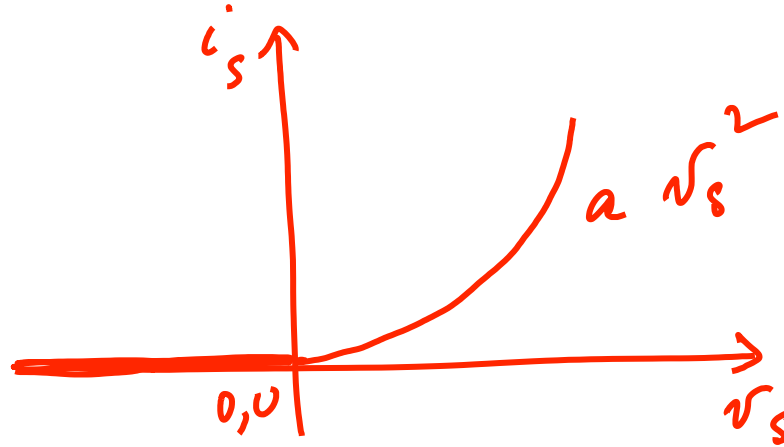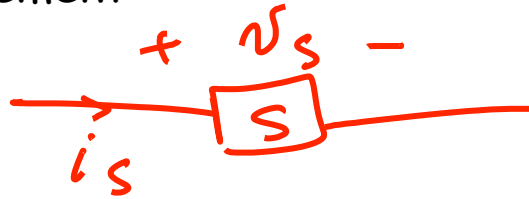

$$\left. \begin{aligned} i_s &= a v_s^2 \\ &\text{for } v_s \geq 0 \end{aligned} \right\}$$
$$= 0 \quad \text{for } v_s < 0$$

Non-Linear Elements

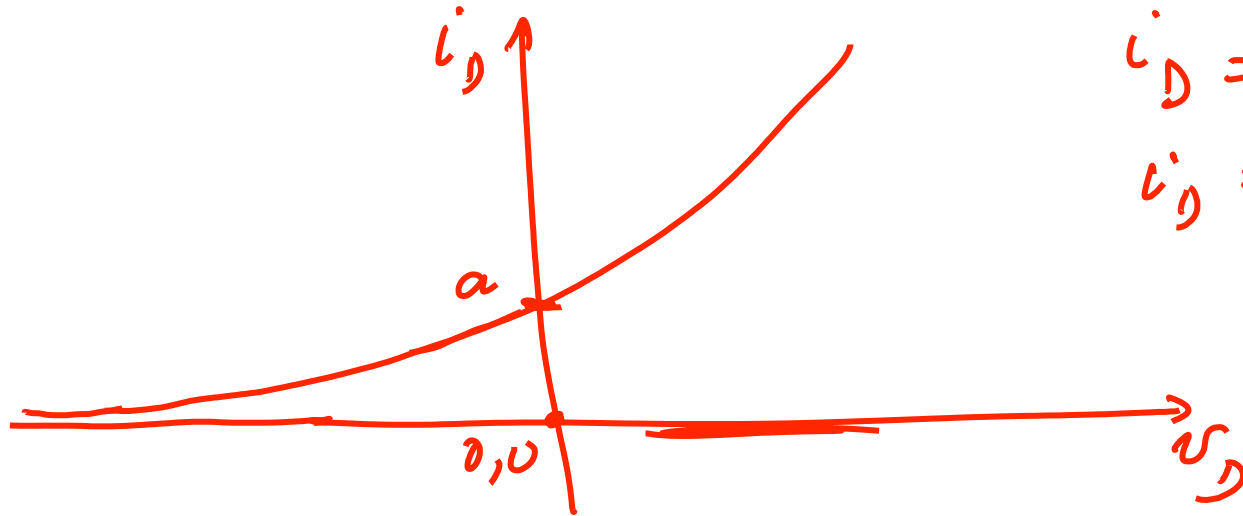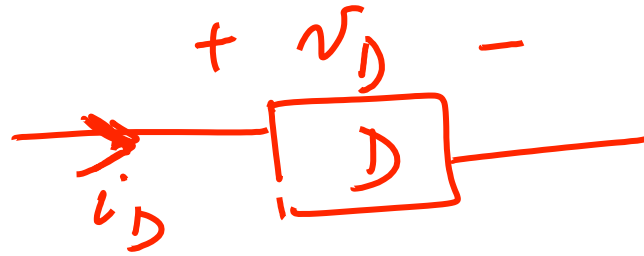Hypothetical nonlinear device
(ExpoDweeb ☺)




$$i_D = a \cdot e^{b v_D}$$
$$i_D = a \text{ for } v_D = 0$$


(Curiously, this funky device supplies power when v_D is negative!)

How do we analyze nonlinear circuits


For example:

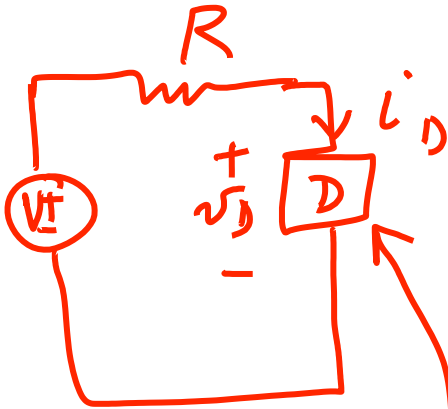

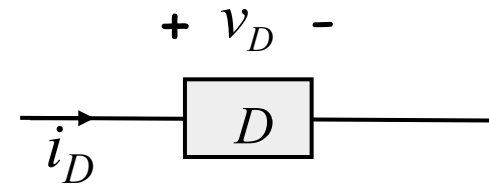
hypothetical
nonlinear
device, the
exponential!



$$\underline{i_D = ae^{bv_D}}$$

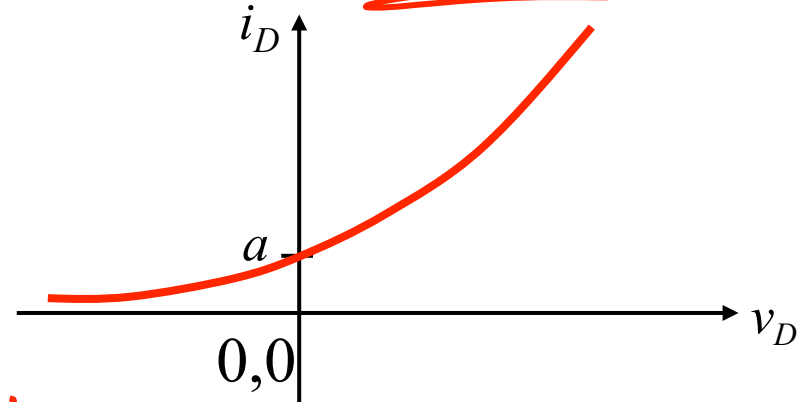


Quick Aside: Note this Key Circuits Hack

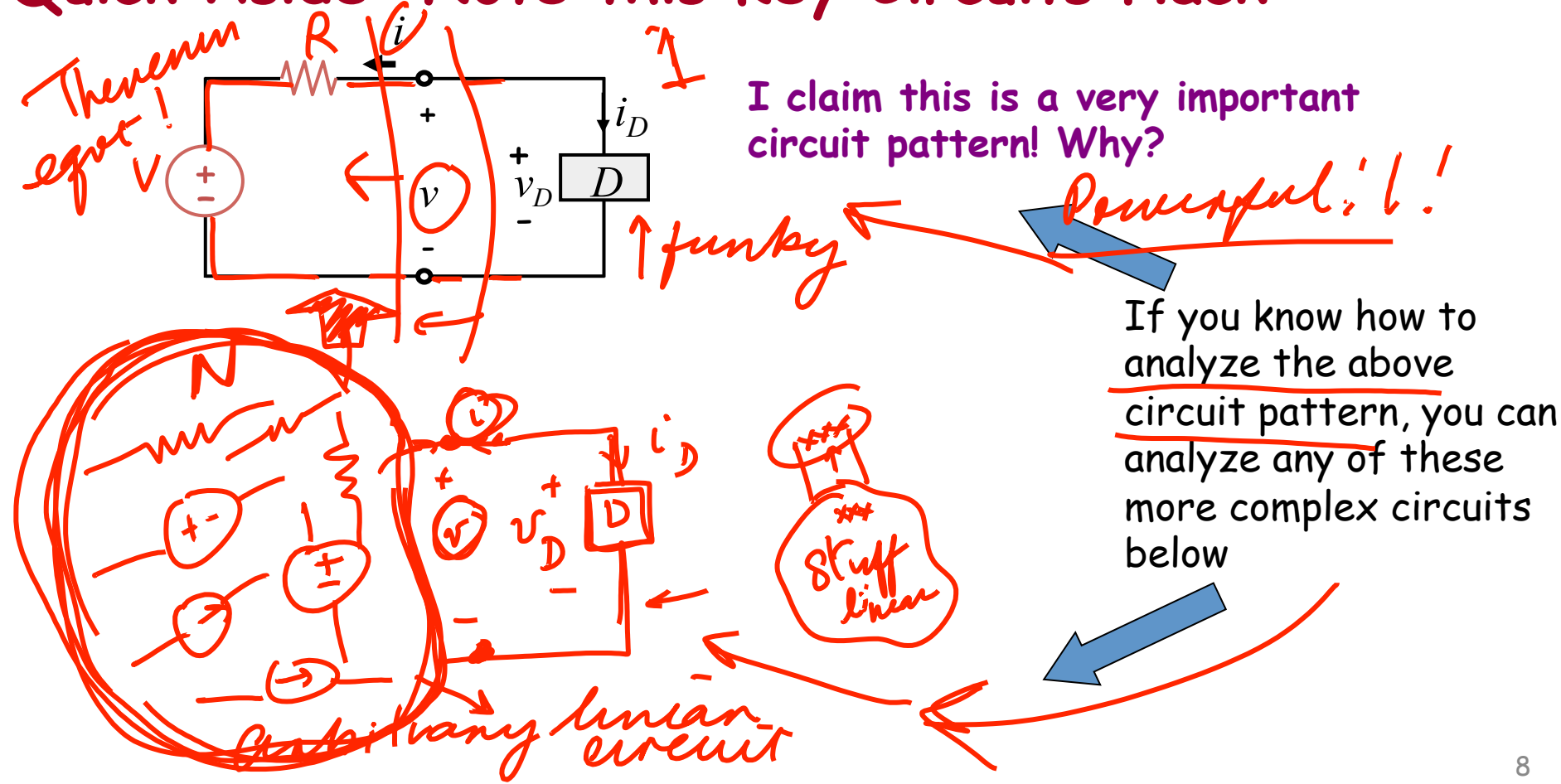

Quick Aside: Note this Key Circuits Hack

Thevenin Trick

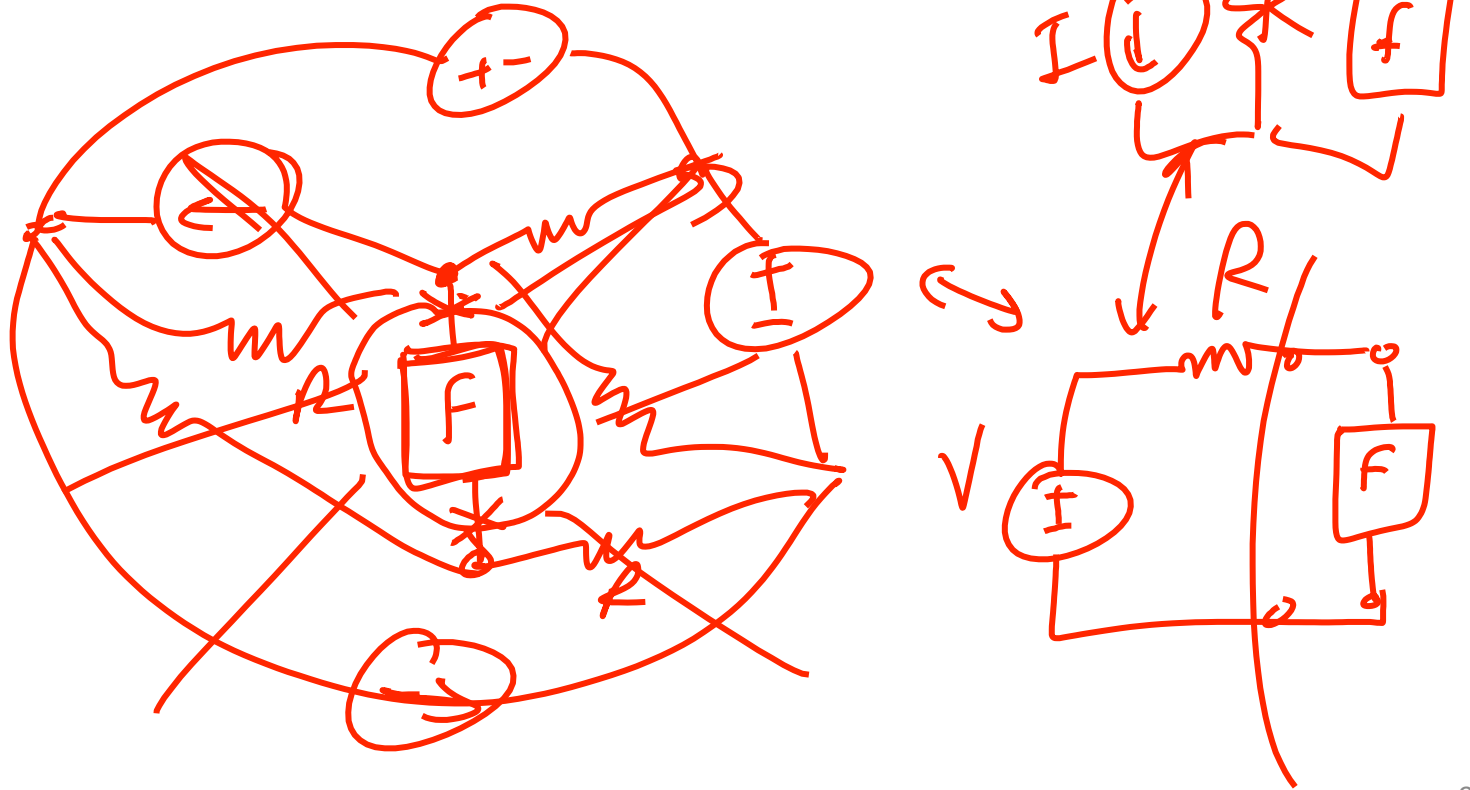

Method 1: Analytical Method

Using the node method,

(remember the node method applies for linear or nonlinear circuits)


$$\frac{v_D - V}{R} + i_D = 0 \quad \text{--- (1)}$$

2 unknowns
2 equations

~~$i_D = a e^{bv_D}$~~

$$i_D = a e^{bv_D} \quad \text{--- (2)}$$

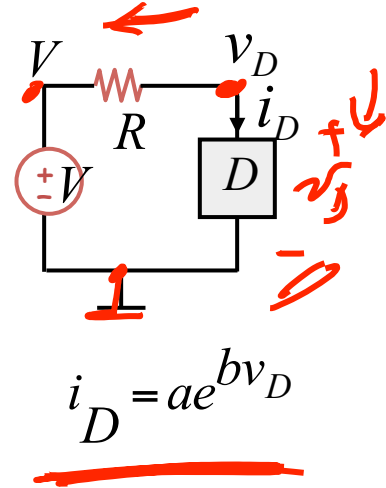Solve by
- trial and error
- numerical techniques



Solve by trial and error

$$\frac{v_D - V}{R} + i_D = 0 \quad (1)$$

$$i_D = a e^{b v_D} \quad (2)$$


$$\frac{v_D - V}{R} + a e^{b v_D} = 0$$

E.g., for $V=1V$, $R=1\text{ Ohm}$, $a=1/4\text{ A}$, $b=1V^{-1}$

$$v_D = V - R a e^{b v_D}$$

$$i_D = a e^{b v_D}$$

Anal. trial method

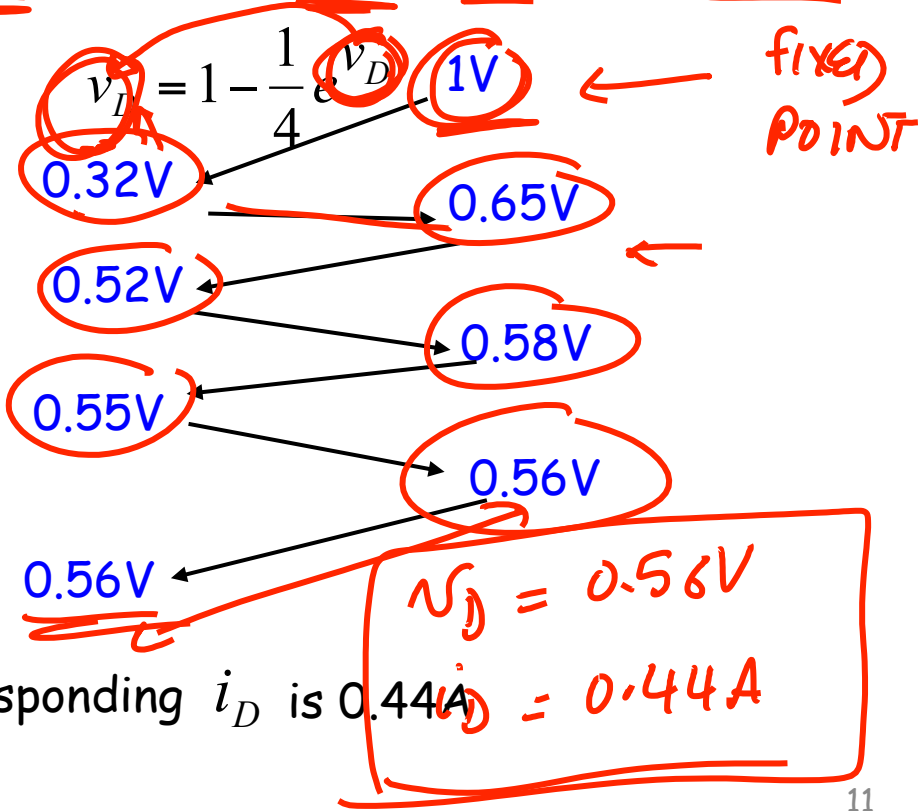

Method 2: Graphical Method

Using the node method

$$\frac{v_D - V}{R} + i_D = 0$$


$$i_D = ae^{bv_D}$$

①

②

$$i_D = \frac{V}{R} - \frac{v_D}{R}$$

rearrange

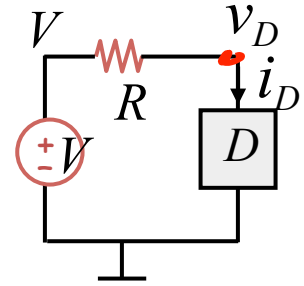

$$i_D = ae^{bv_D}$$


2 unknowns, 2 equations

Can also solve by the graphical method


Method 2: Graphical Method

Notice: the solution satisfies equations (1') and (2)
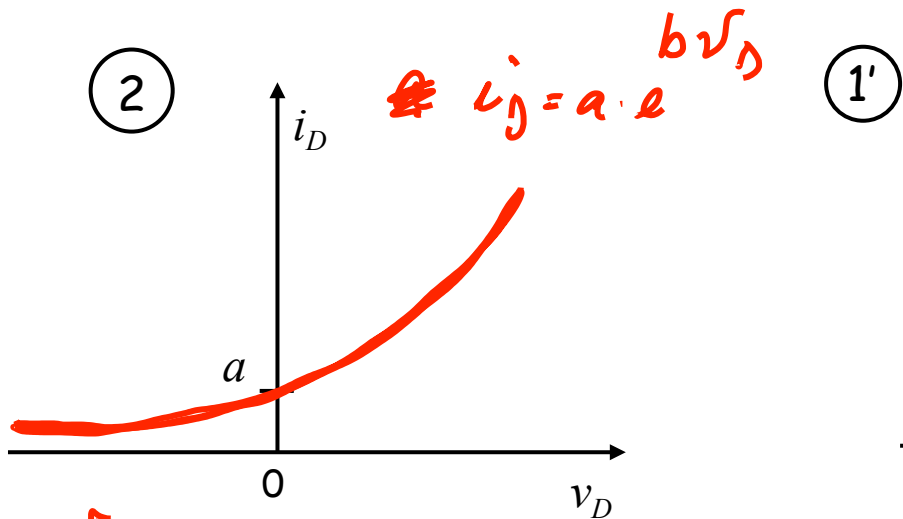
$$i_D = \frac{V}{R} - \frac{v_D}{R} \quad (1')$$
$$i_D = a e^{b v_D} \quad (2)$$



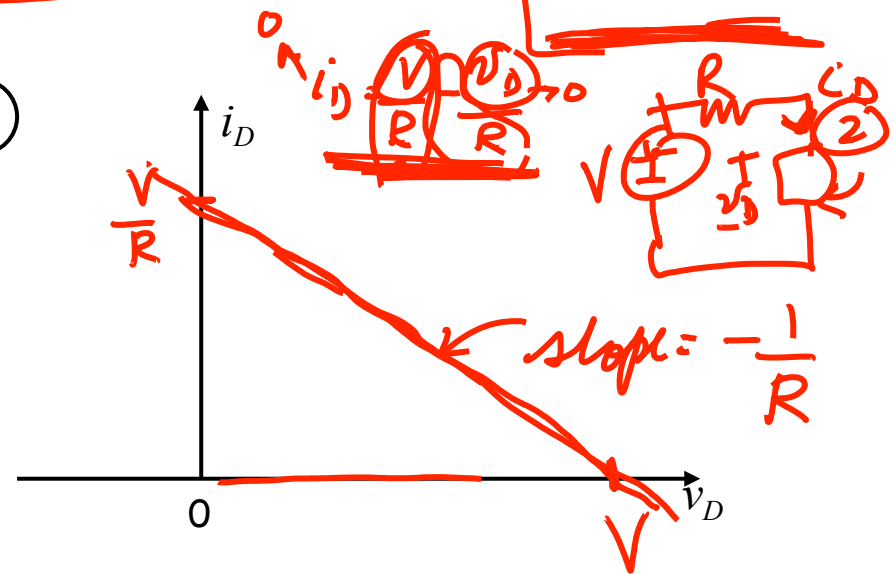Constraint on i_D and v_D imposed by device



Constraint on i_D and v_D imposed by the rest of the circuit (Thevenin equivalent circuit)

Combine the two constraints


E.g., for $V=1V$, $R=1\text{ Ohm}$, $a=1/4\text{ A}$, $b=1V^{-1}$

$$i_D = \frac{V}{R} - \frac{v_D}{R} \quad (1')$$

$$i_D = ae^{bv_D} \quad (2)$$

$$i_D = 1 - v_D \quad (1')$$

$$i_D = \frac{1}{4} e^{v_D} \quad (2)$$

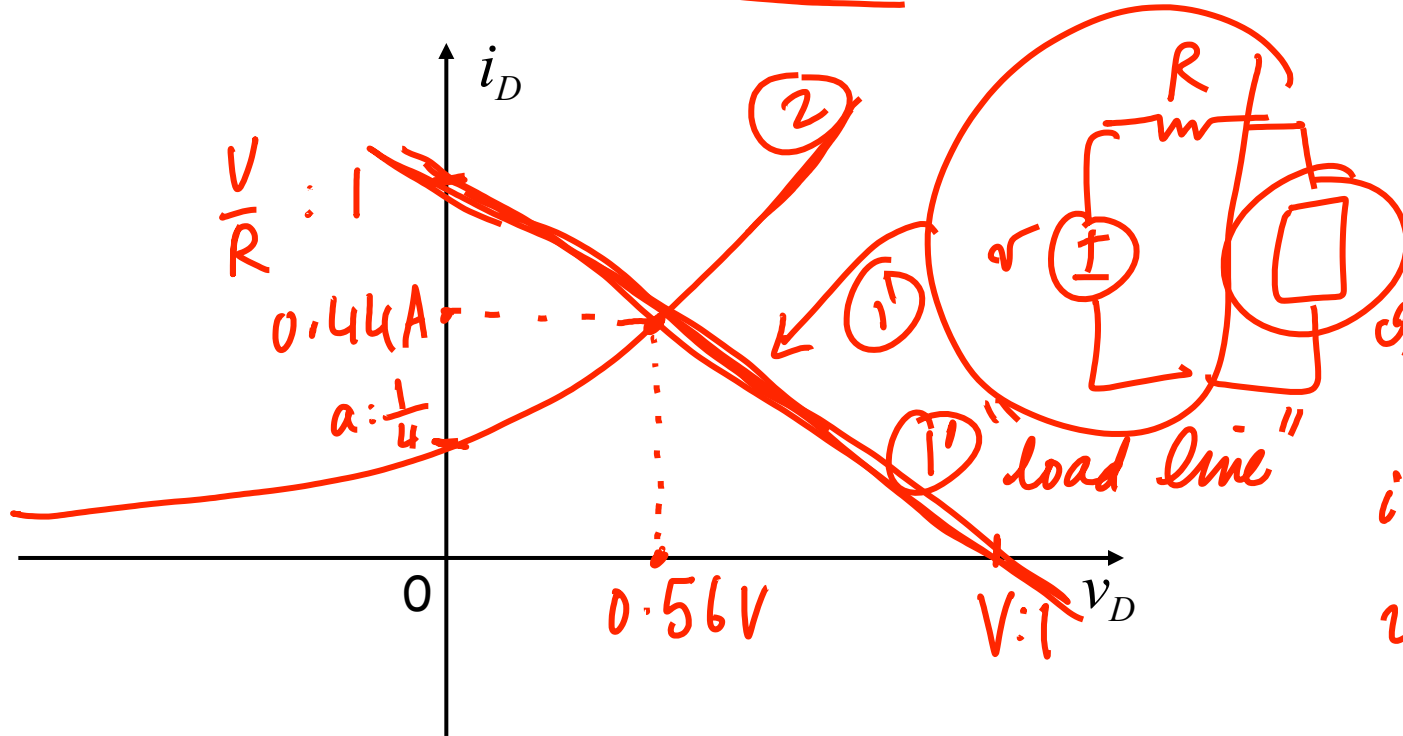

$$i_D = 0.44\text{ A}$$




$$v_D = 0.56\text{ V}$$

Interesting

Combining the two constraints



$$i_D = \frac{V}{R} - \frac{v_D}{R} \quad (1')$$

$$i_D = ae^{bv_D} \quad (2)$$

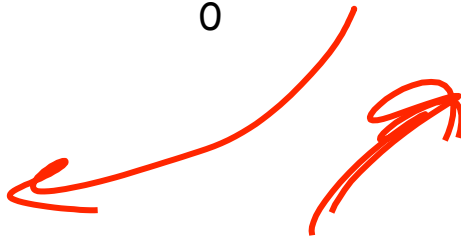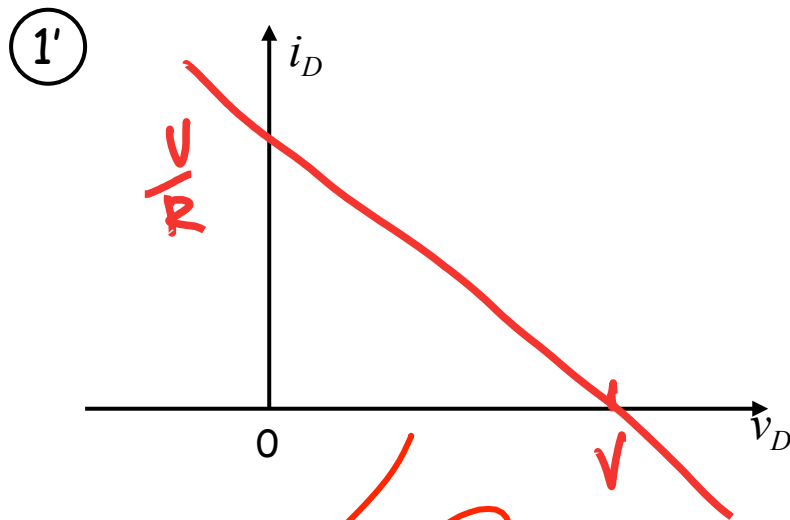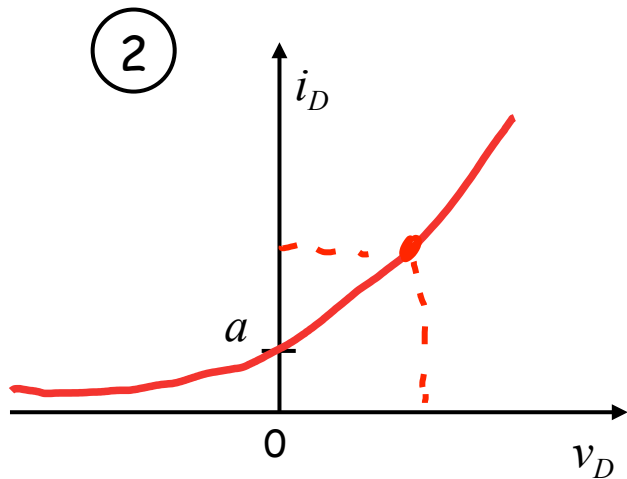

Method 3: Piecewise Linear Method

Insight:

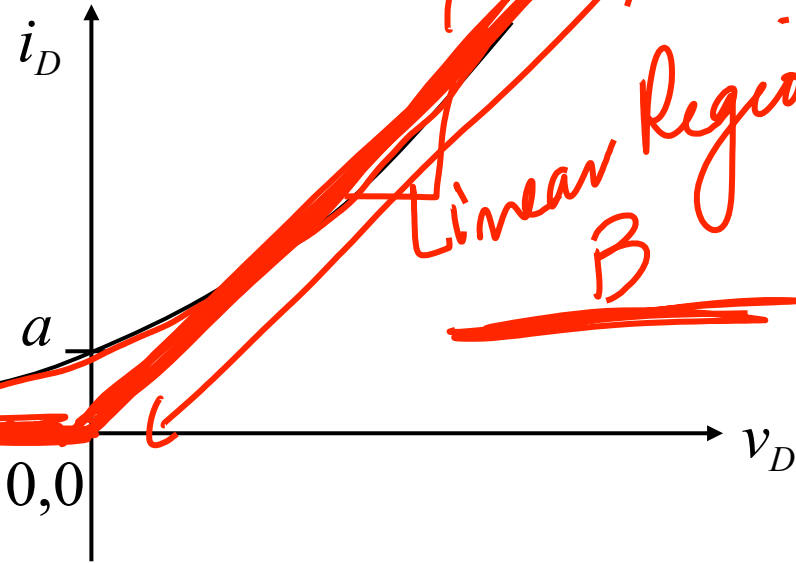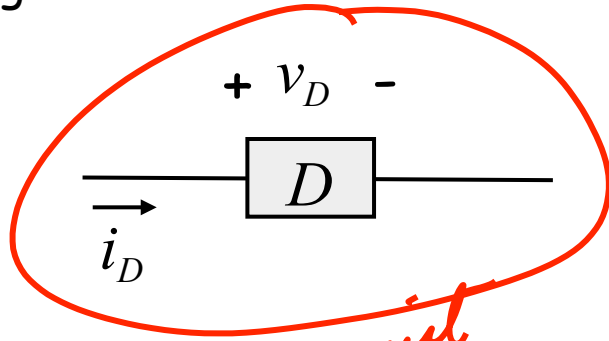

like an open circuit




Linear Region A

- Determine which of the linear regions applies (e.g., region B)
- Solve circuit assuming that linear relation (from region B)

See Sec 4.4 of the text for details and examples

Piecewise Linear Method


For example:

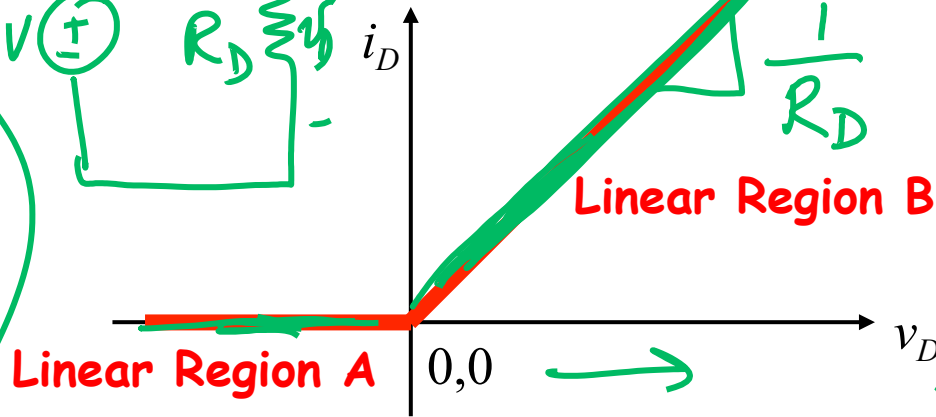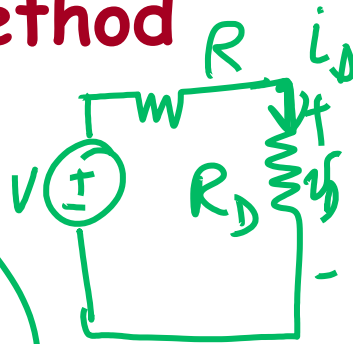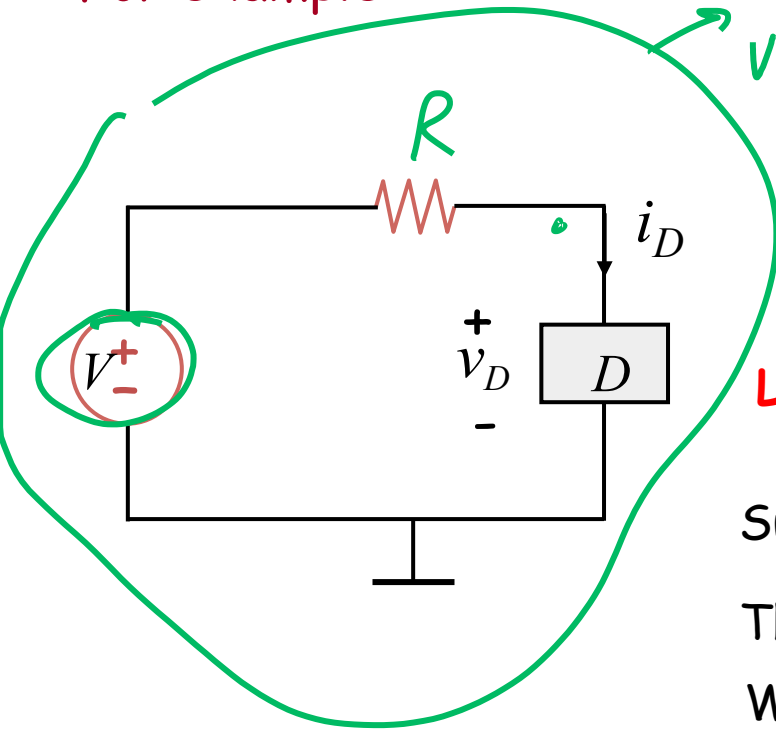

Suppose we are given that V is positive

Then D will operate in Linear Region B

We can replace D in the circuit with a resistance of value $1/R_D$ when D operates in region B

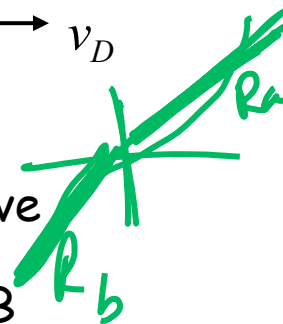


Method 3: Incremental Analysis


Small signal method

(Actually, a disciplined way of using a circuit called small signal method)

Motivation: music over a light beam. Can we pull this off?


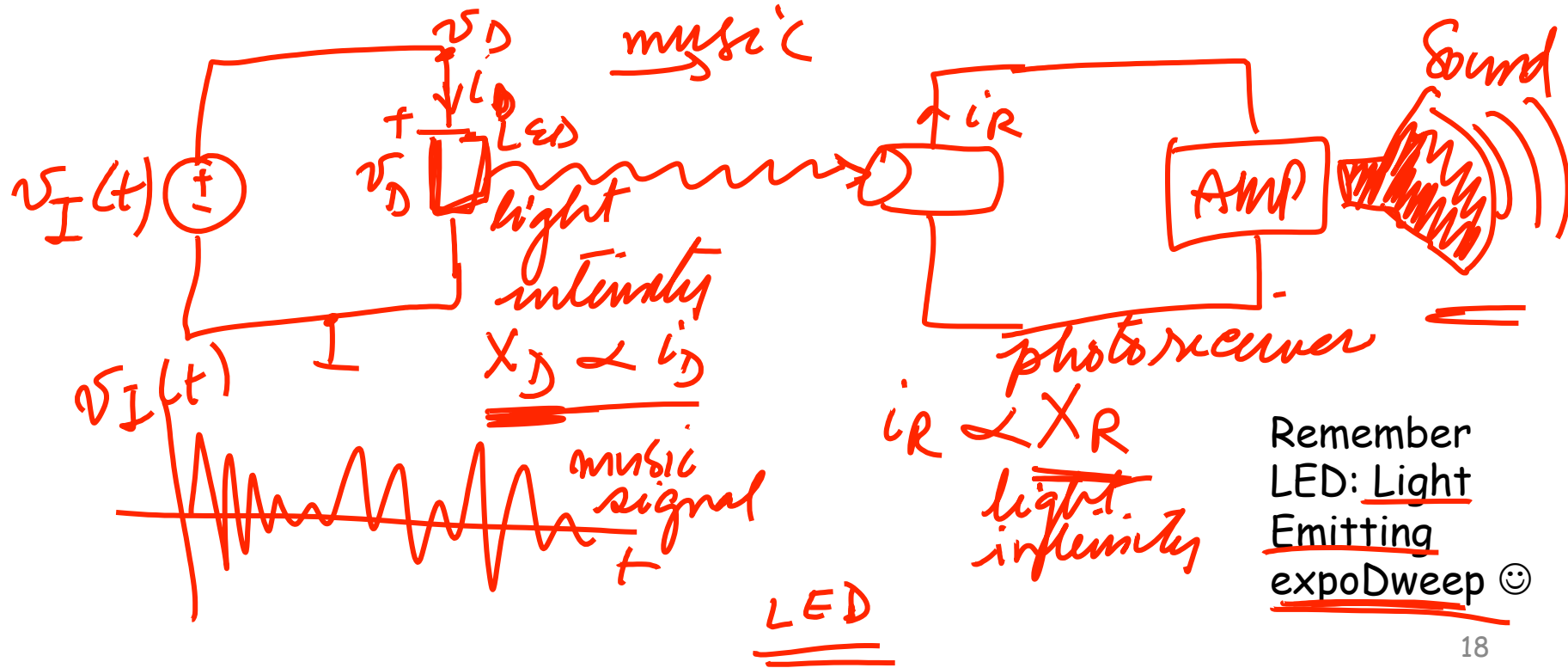


Method 3: Incremental Analysis


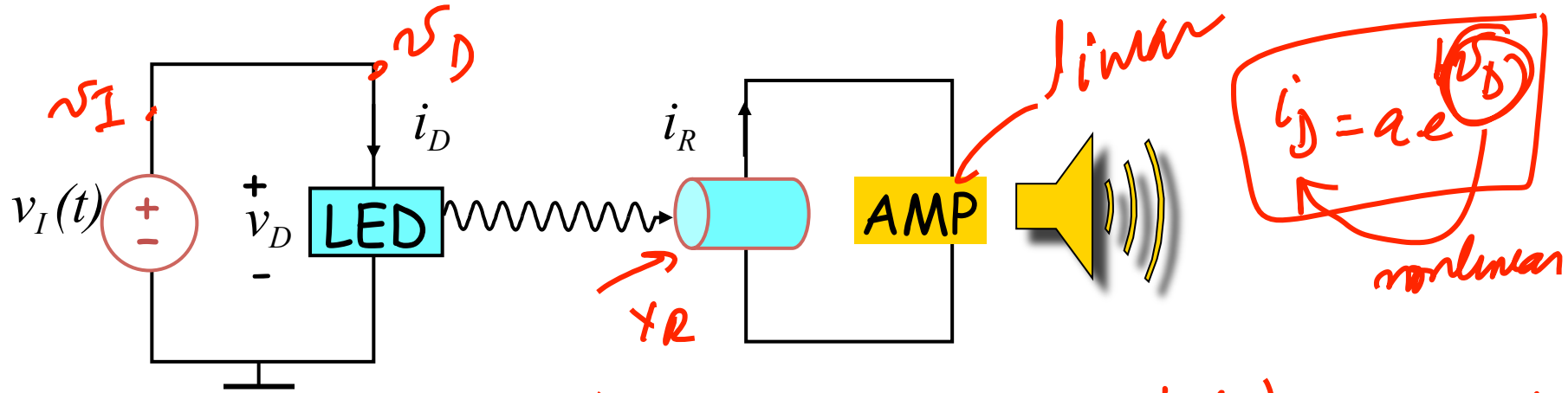


$v_I(t) \Rightarrow i_D(t) \xrightarrow{\text{light}} i_R(t) \rightarrow \text{Sound}$
 $\sqrt{2}I = \sqrt{2}D$ non linear!
problem $\rightarrow$ will result in distortion
linear

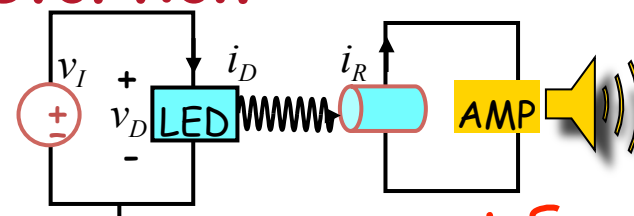
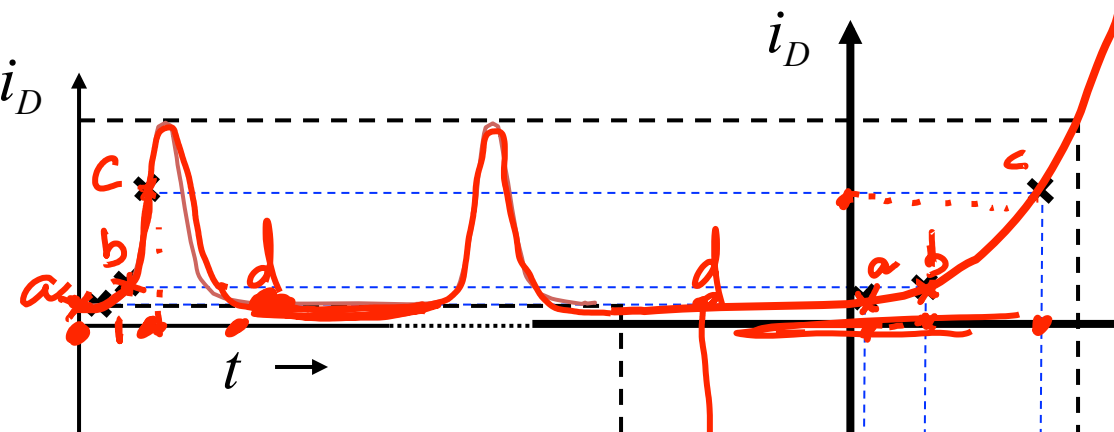
Problem: The LED is nonlinear $\rightarrow$ distortion



$i_D = a e^{b \sqrt{v_D}}$

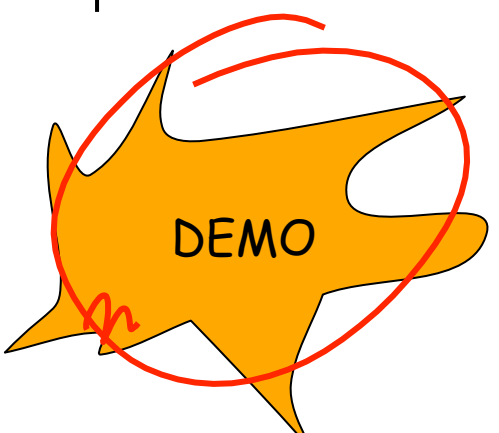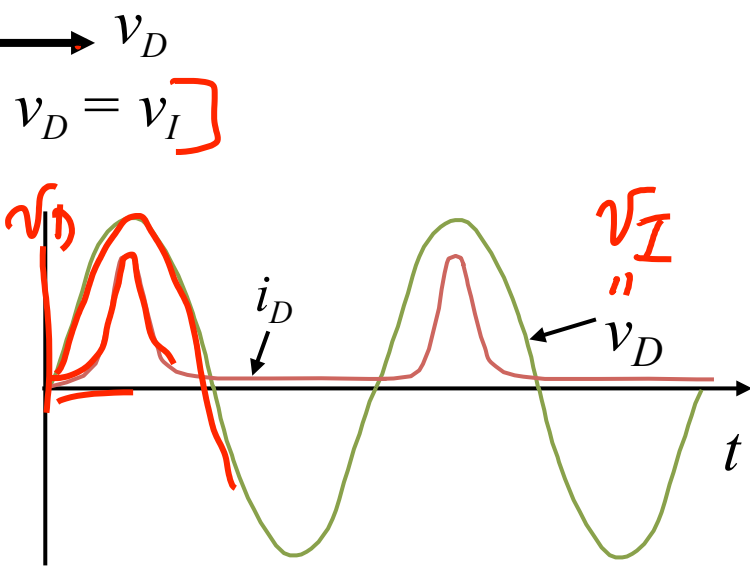

If only the LED were linear ...

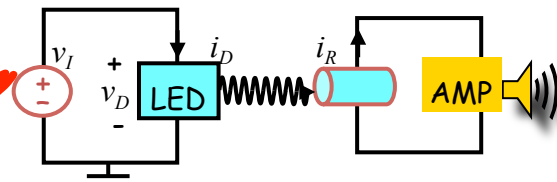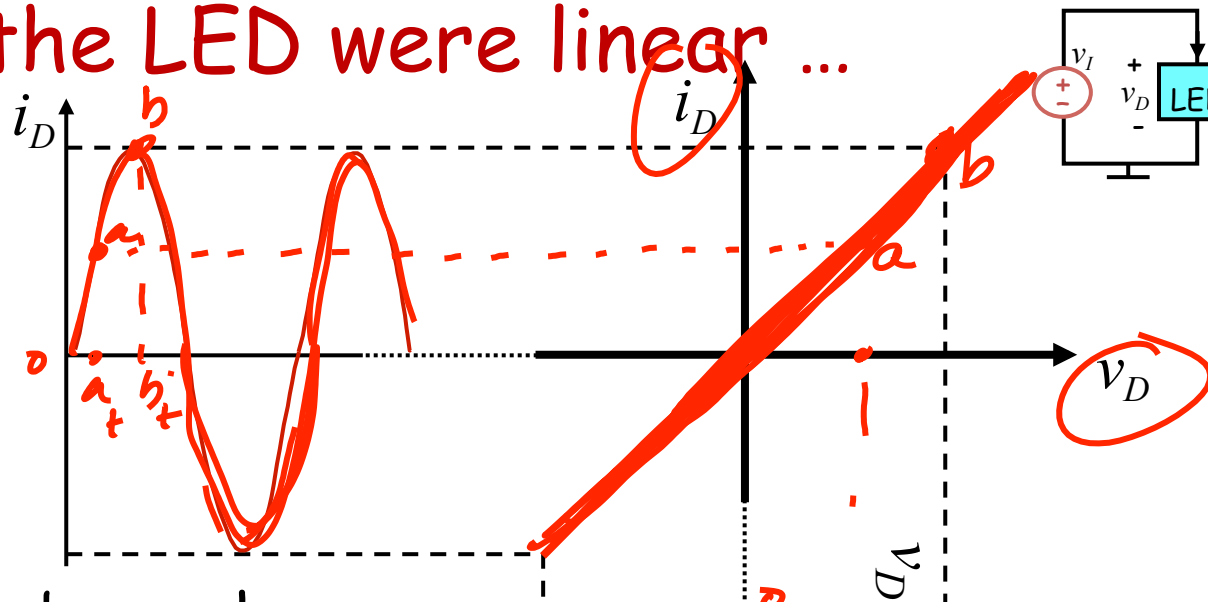

it would've been ok.

What do we do?
Zen is the answer
... next sequence!

