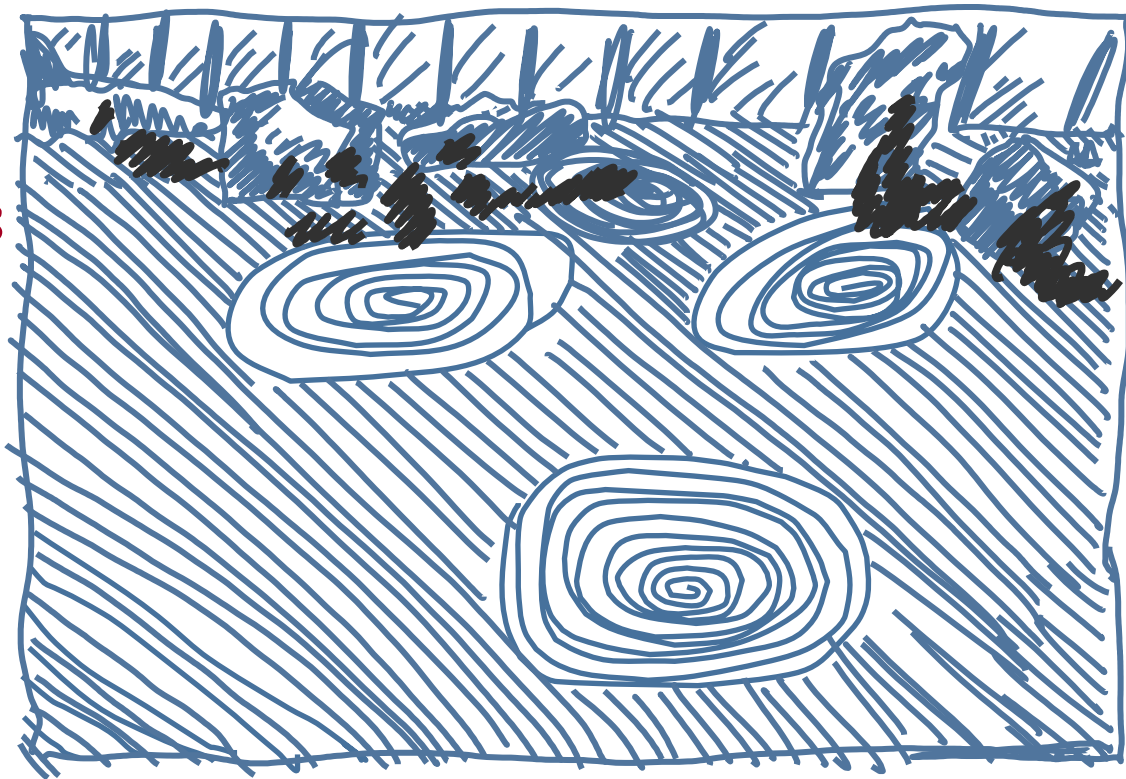


## Incremental Analysis

*Small signal  
trick*




# Review

## The 6.002x world

Linear

Superposition  
Thevenin, Norton

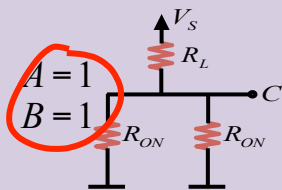

Lumped Circuit Abstraction

KVL/KCL

Node

Composition

Nonlinear

Analytical  
Graphical


Small Signal Model

Digital

$A$

$B$

For fixed input values ...

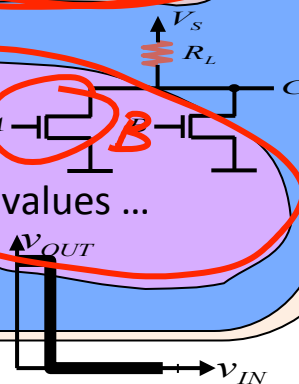

## Nonlinear Analysis

- ▶ Analytical method
- ▶ Graphical method
- ▶ Piecewise Linear method

Today


- ▶ Incremental analysis or small signal method

**Reading: Section 4.5**

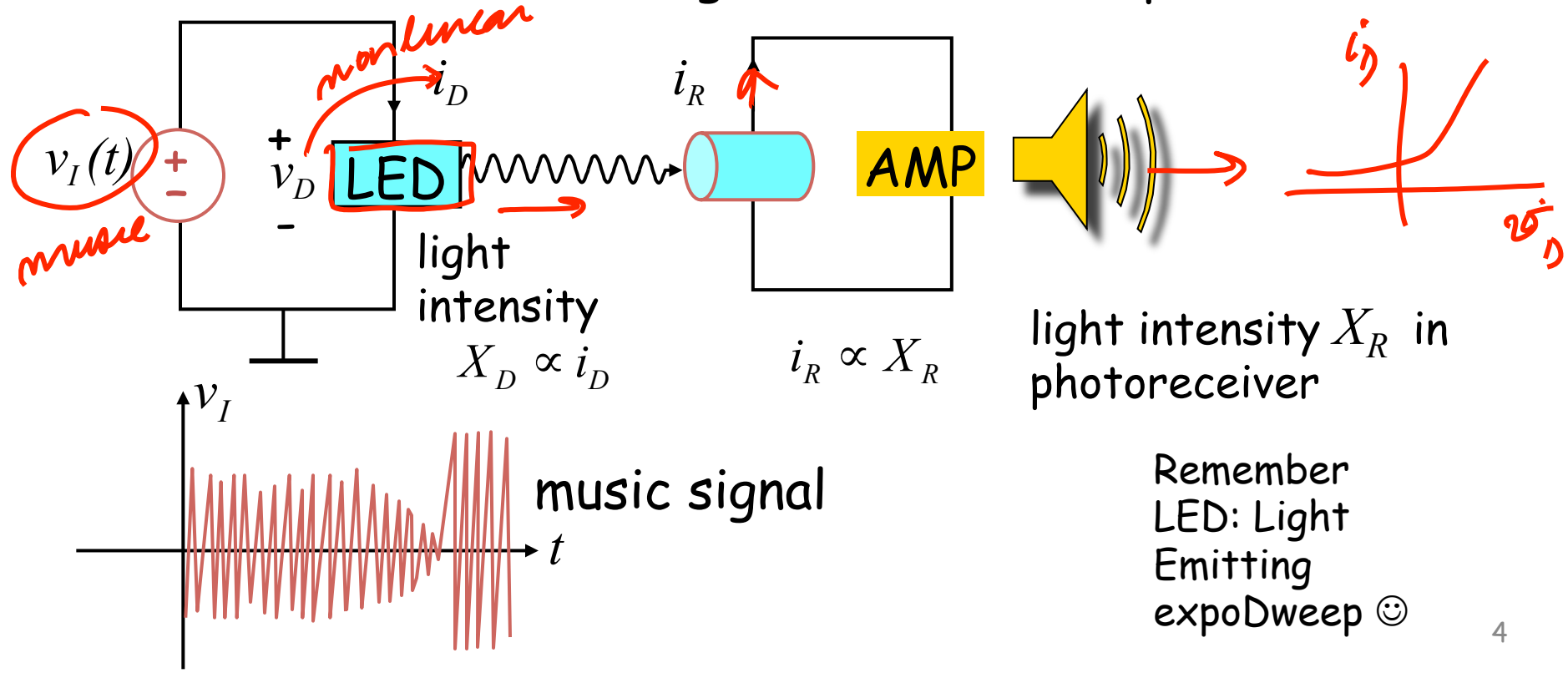
# Method 3: Incremental Analysis

(Actually a particular disciplined use of a circuit)


Motivation: music over a light beam. Can we pull this off?





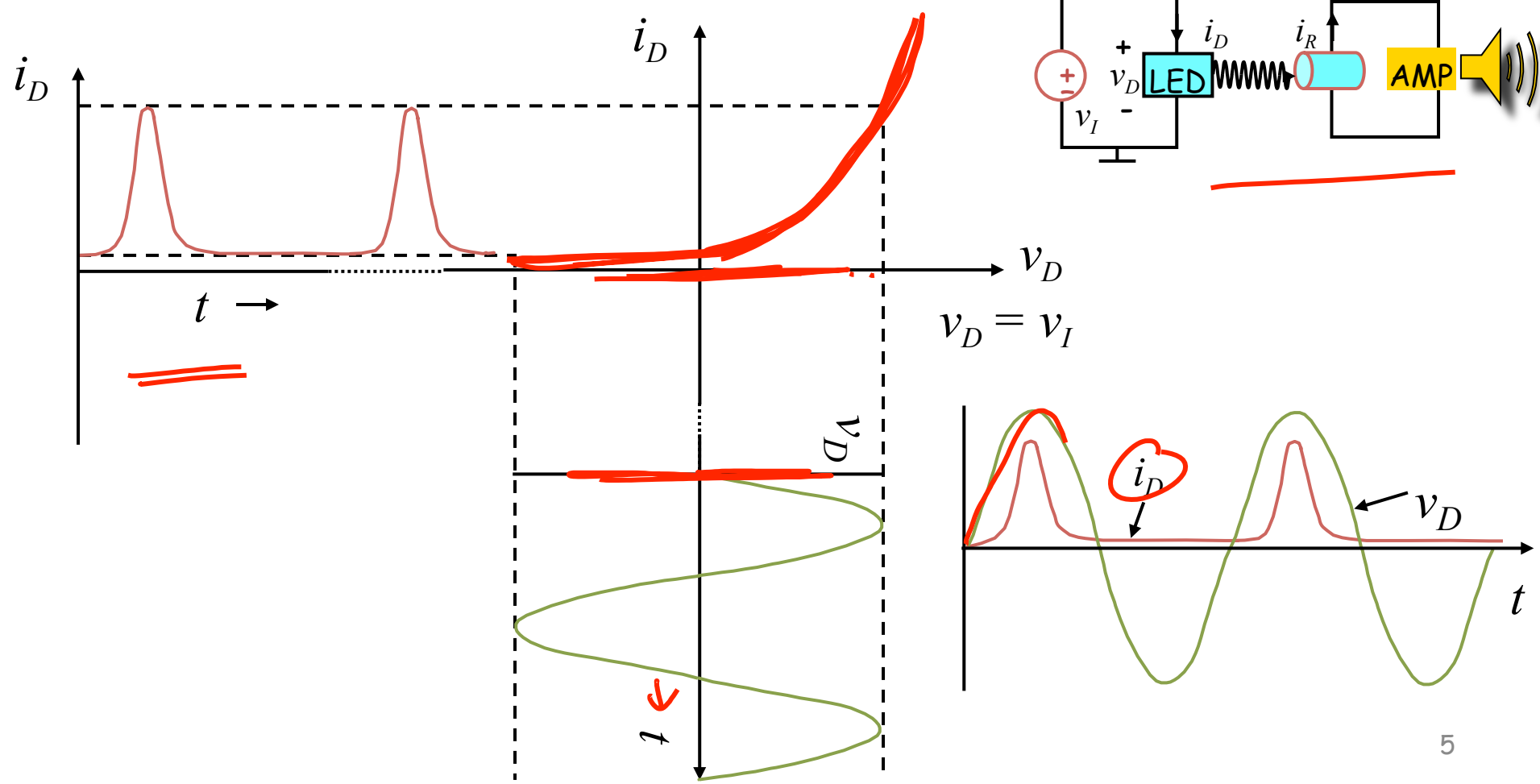
# Problem: The LED is nonlinear $\rightarrow$ distortion



# Problem: The LED is Nonlinear

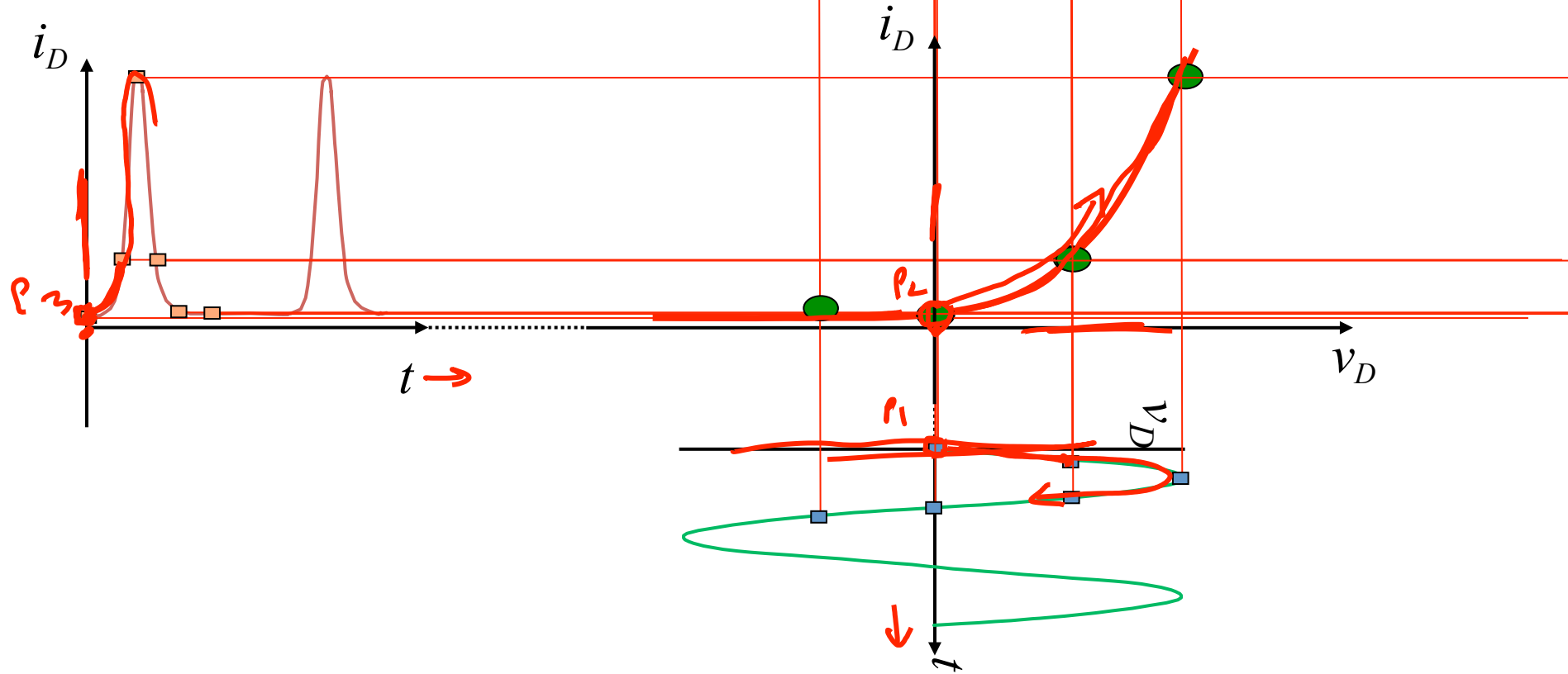


# Insight

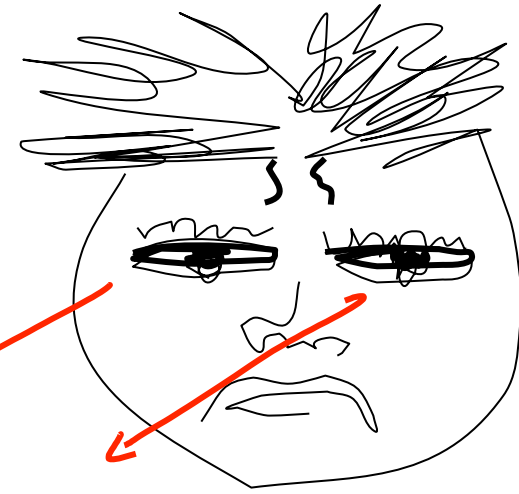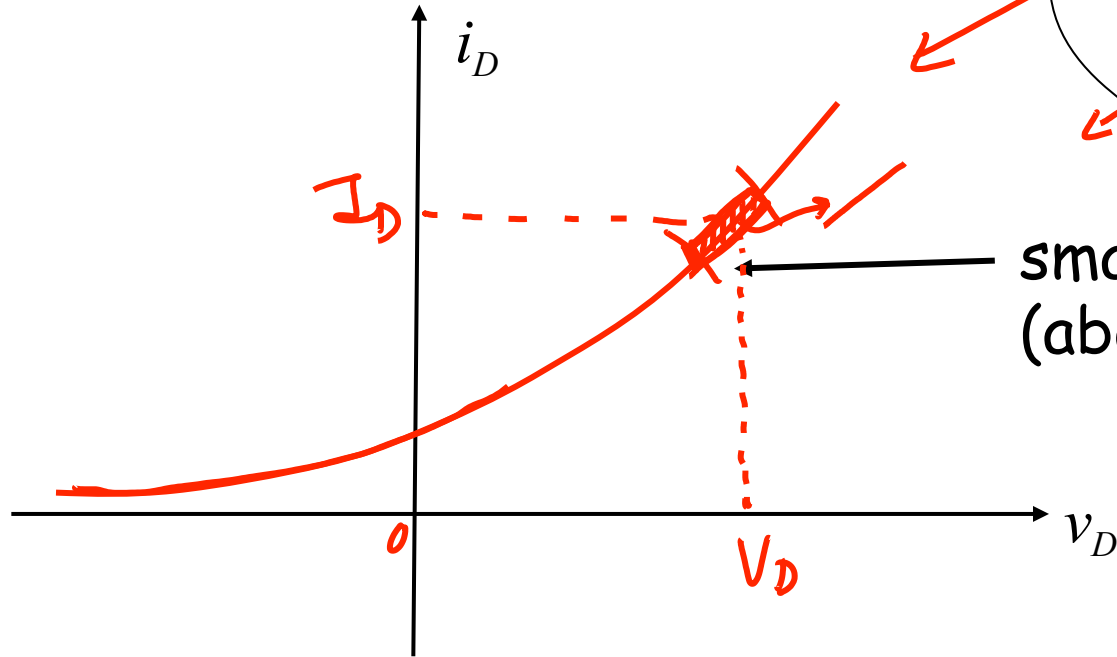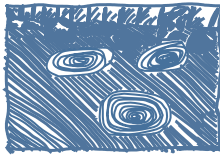


small region looks linear  
(about some given  $V_D$ ,  $I_D$ )

# Imagine

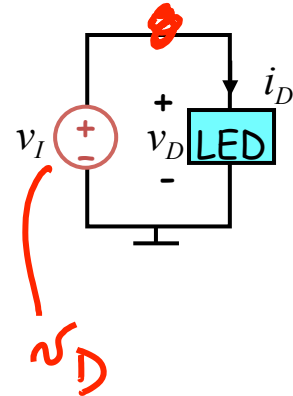




very small  $i_D$

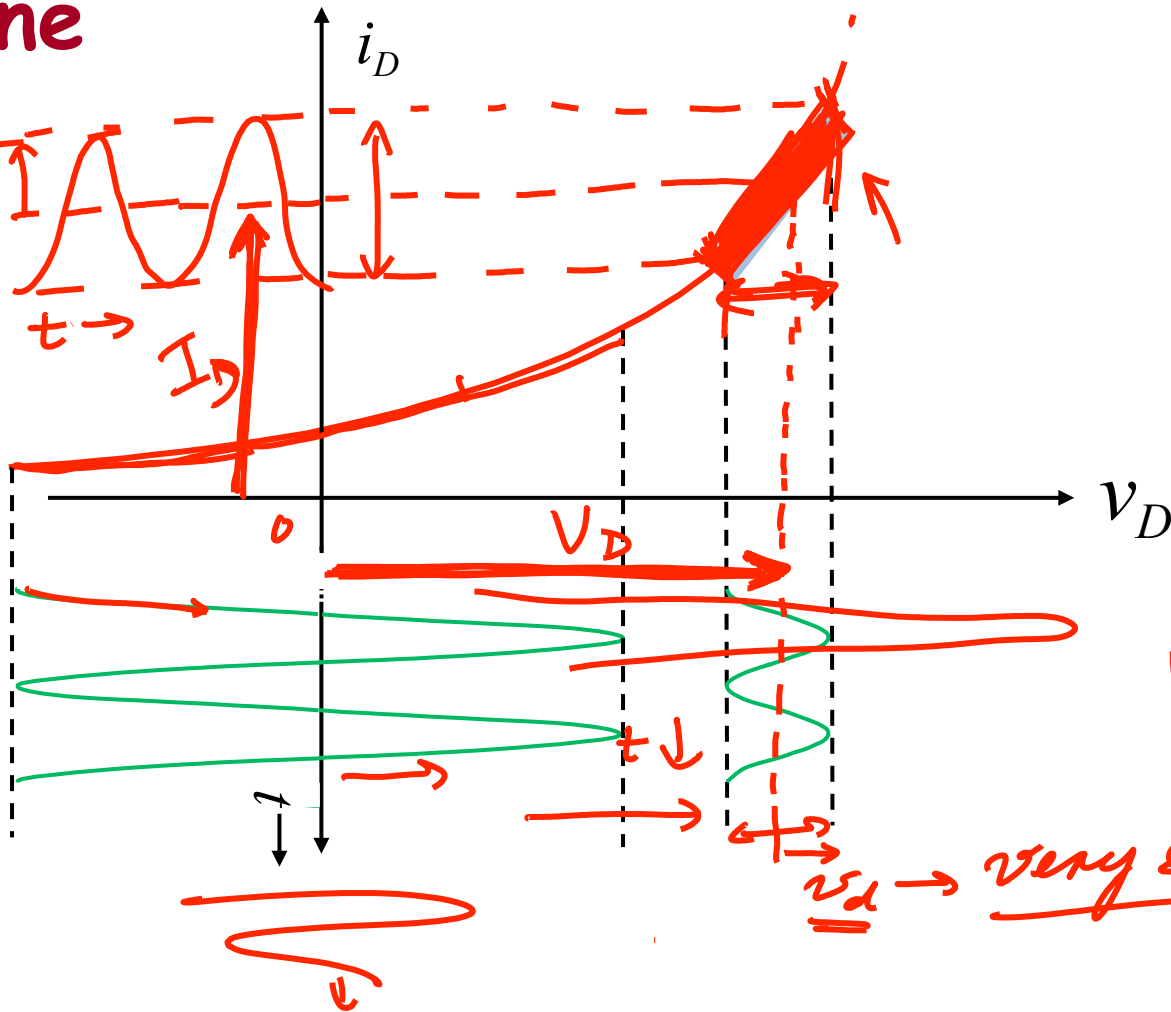

$v_D$  Boost  
and  
Shrink  
 $v_d$



# How to implement this trick

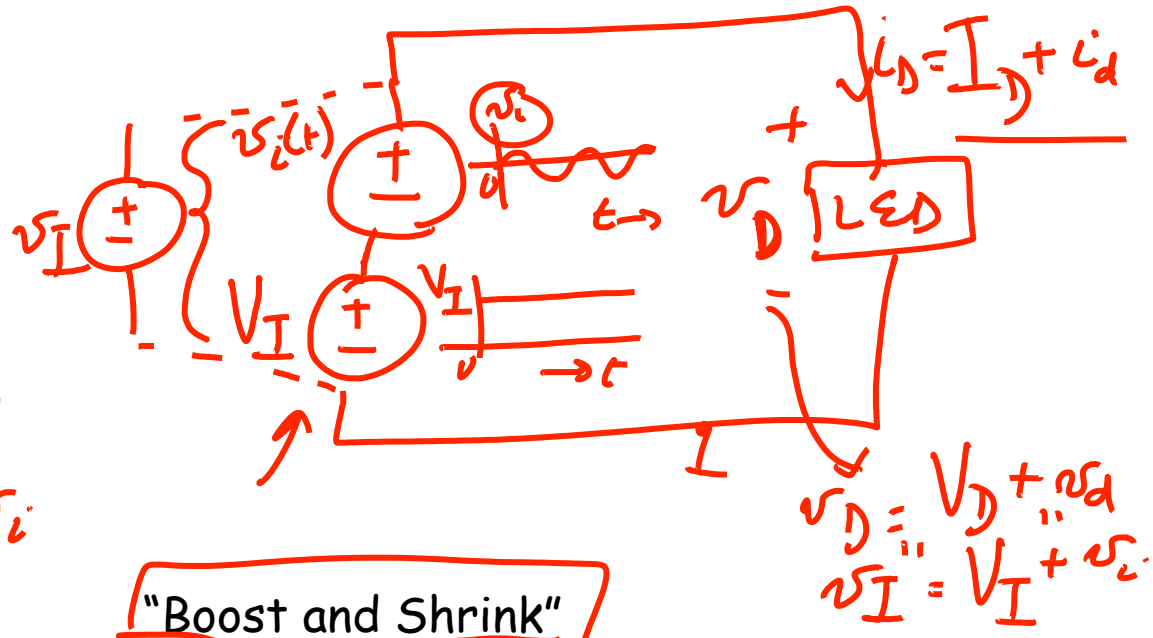
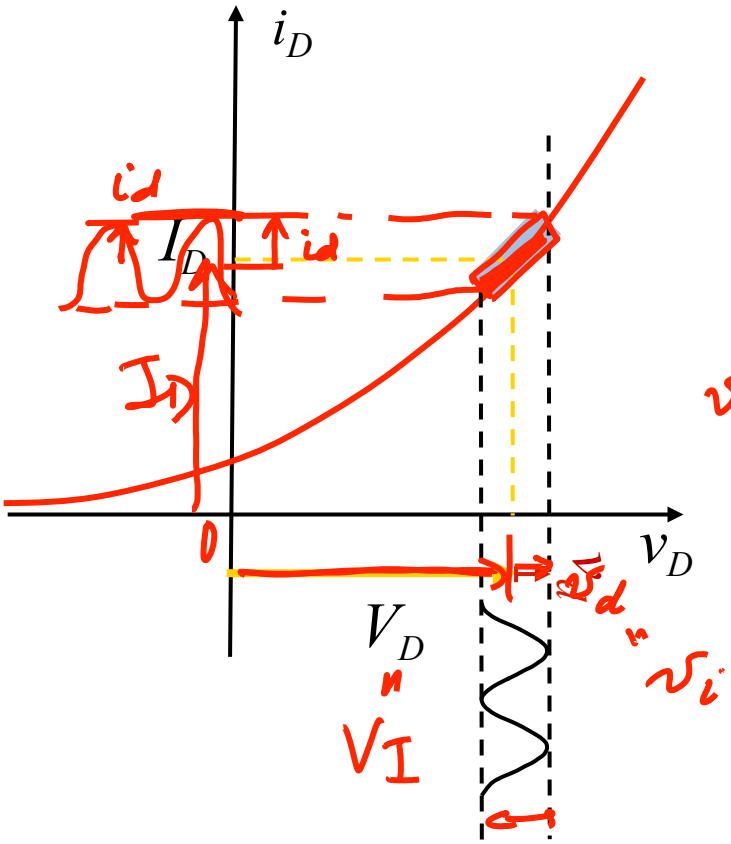
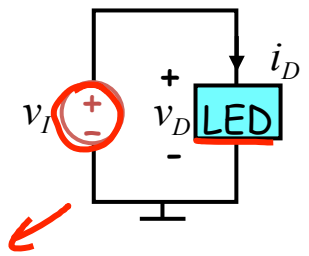


"Boost and Shrink"

- Shrink signal of interest  $v_i$
- Add DC offset to it  $V_I$

# Result

Small signal trick

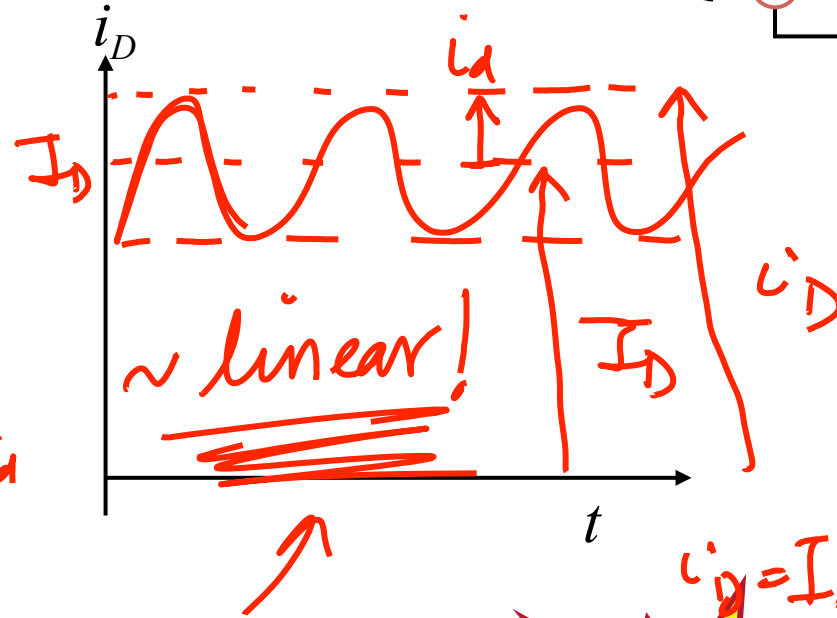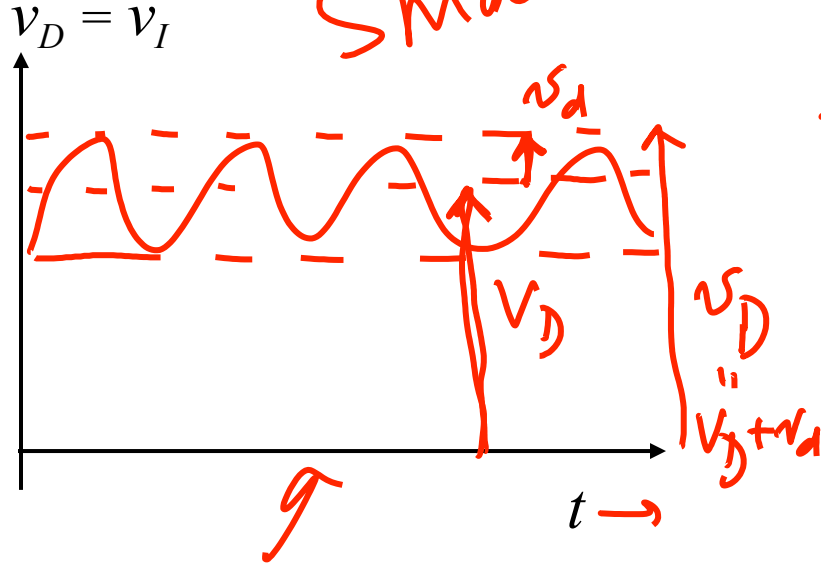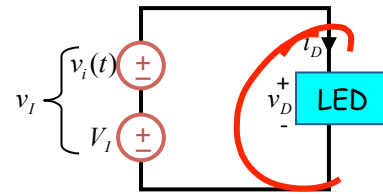

So, this is really a very clever and disciplined way of using a circuit so that we can get a more or less linear response out of a nonlinear circuit

$i_D = I_D + i_d$   
**Demo**

# The incremental method: (or small signal method)

1. Operate at some DC offset or bias point  $\underline{V_D, I_D}$ .
2. Superimpose small signal (music) on top of  $V_D$ .  $v_d$
3. Response  $i_d$  to small signal  $v_d$  is approximately linear.

Notation

$$i_D = I_D + i_d$$

total variable      DC offset      small superimposed signal

# What does this mean mathematically?

Or, why is the small signal response linear? ←

we replaced  $i_D = f(v_D)$  ← nonlinear

$$v_D = \underbrace{V_D}_{\text{large DC}} + \underbrace{\Delta v_D}_{\text{small increment about } V_D}$$

Using Taylor's Expansion to expand  $\underline{f(v_D)}$  near  $\underline{v_D = V_D}$ :

$$i_D = \underline{f(V_D)} + \left. \frac{df(v_D)}{dv_D} \right|_{v_D = V_D} \boxed{\Delta v_D} + \frac{1}{2!} \left. \frac{d^2 f(v_D)}{dv_D^2} \right|_{v_D = V_D} \Delta v_D^2 + \dots$$

Neglect higher order terms  $\rightarrow v_D$  small

# Why is the small signal response linear?

$i_D \approx f(V_D) + \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \Delta v_D + \dots$

$i_D = f(v_D)$

constant w.r.t.  $\Delta v_D$       constant w.r.t.  $\Delta v_D$  slope at  $V_D, I_D$

higher order term

(X):

$I_D + \Delta i_D \approx f(V_D) + \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \Delta v_D$

equate DC & time varying component

$I_D = f(V_D)$

→ operating point

$\Delta i_D = \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \Delta v_D$

const. w.r.t.  $\Delta v_D$

# Why is the small signal response linear?

(X):

$$I_D + \Delta i_D \approx f(V_D) + \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \cdot \Delta v_D$$

DC

$I_D = f(V_D)$   
operating point

time varying part


$$\Delta i_D = \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \cdot \Delta v_D$$

const. wrt  $\Delta v_D$

so  $\Delta i_D \propto \Delta v_D$

$\Delta i_D \rightarrow i_d$   
 $\Delta v_D \rightarrow v_d$

Incremental response is linear

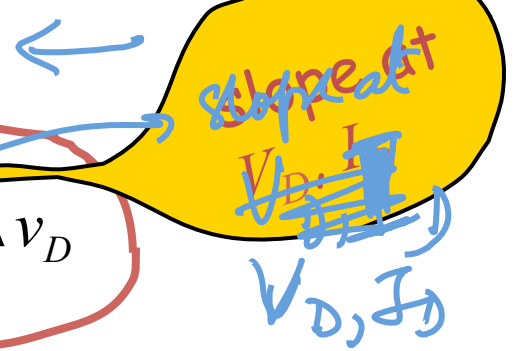

In our example

$$i_D = f(v_D) = a e^{b v_D} \quad \textcircled{X} : I_D + \Delta i_D \approx f(V_D) + \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \cdot \Delta v_D$$

From  $\textcircled{X}$ :  $I_D + i_d \approx a e^{b V_D} + a \cdot b e^{b V_D} \cdot v_d \rightarrow I_D!$

$$\approx \underbrace{a e^{b V_D}}_{I_D} + \underbrace{a e^{b V_D}}_{I_D} \cdot b \cdot v_d$$

Equating DC and incremental terms

$$\boxed{\begin{matrix} \text{DC} & b V_D \\ I_D = a e \end{matrix}}$$

↓  
operating point  
aka DC offset  
aka bias point

Incremental terms

$$i_d = \underbrace{a e^{b V_D}}_{I_D} \cdot b \cdot v_d$$

$$\boxed{i_d = I_D \cdot b \cdot v_d}$$

constant

small signal response  
is linear!


# Graphical interpretation

→  $I_D = a e^{bV_D}$  → operating point


→  $i_d = I_D \cdot b \cdot v_d$  → slope at  $V_D, I_D$

$$i_D = f(v_D)$$

$$i_D = a e^{b v_D}$$

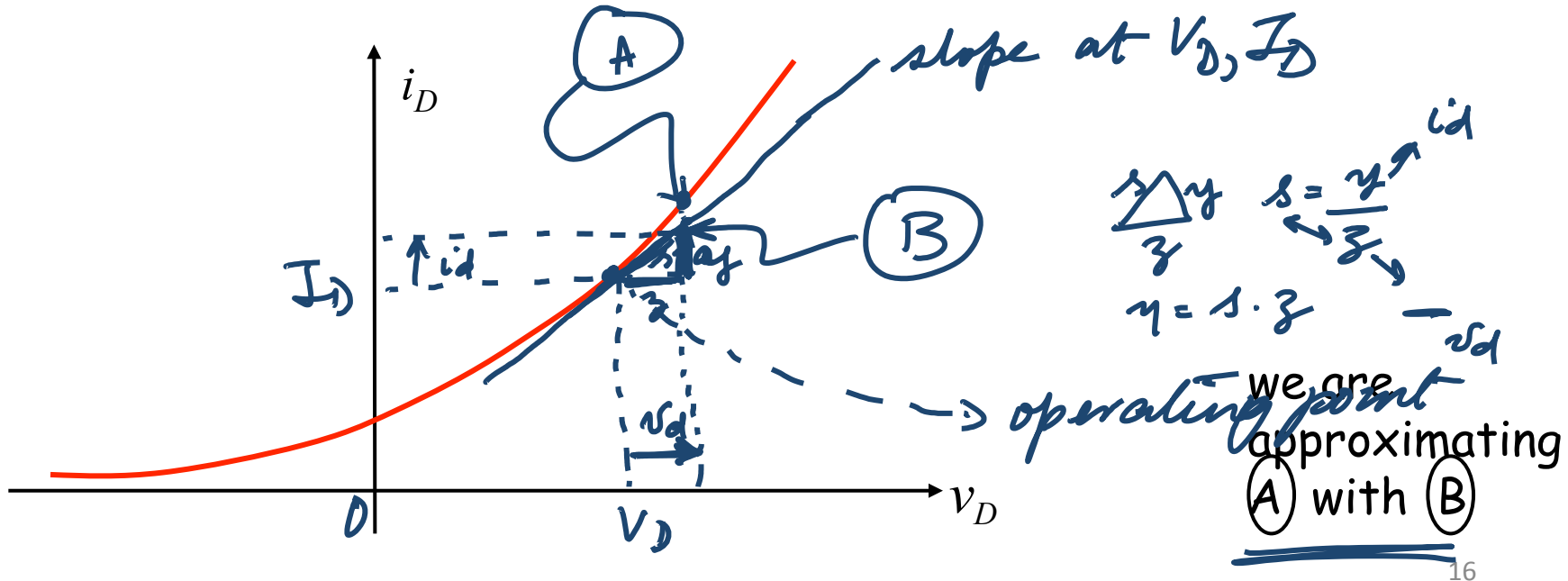



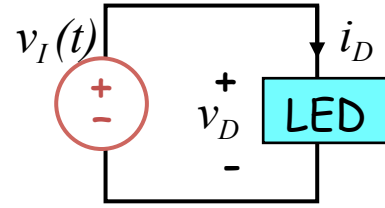

$$v_D = f(v_D) = a e^{bV_D}$$

$$I_D = a e^{bV_D}$$


$$i_d = I_D \cdot b \cdot v_d$$

We studied the small signal

- graphically ←
- mathematically ←
- Next, circuit view


# A circuit view of the small signal model

Large signal circuit:

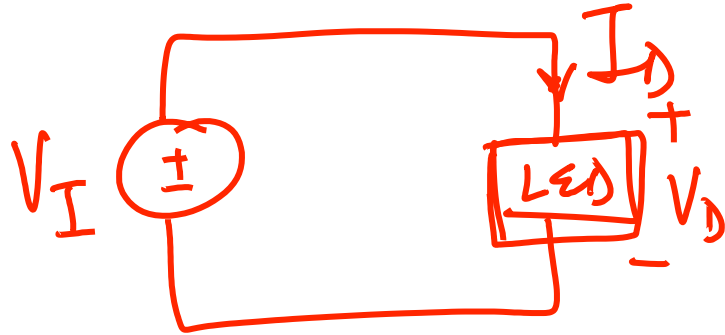

$$I_D = a e^{bV_D}$$

some nonlinear system

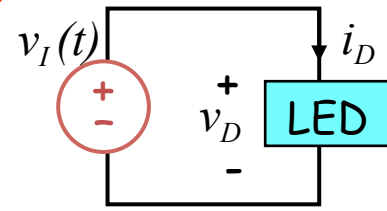

$$v_D = f(v_D) = a e^{bV_D}$$

$$\Rightarrow I_D = a e^{bV_D}$$

$$\Rightarrow i_d = I_D \cdot b \cdot v_d$$

Small signal response:

$$\rightarrow i_d = \underbrace{I_D \cdot b}_{\text{constant}} v_d$$

$$R = \frac{1}{I_D \cdot b}$$

circuit interpretation  
of the equation

For small signals, device behaves like a resistor!


Where did you see  
 $i = \text{constant} \times v$   
before?

$$R = \frac{1}{\frac{df(v_D)}{dv_D}}$$


$v_D = V_D$

# So, We Can Build a Small Signal Circuit


Large signal circuit:

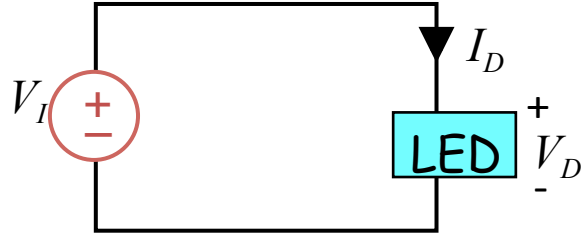

Small signal response:

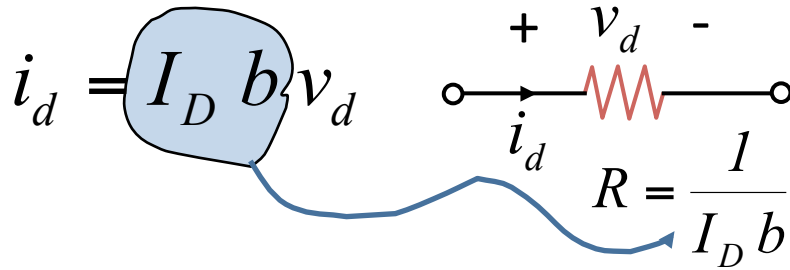

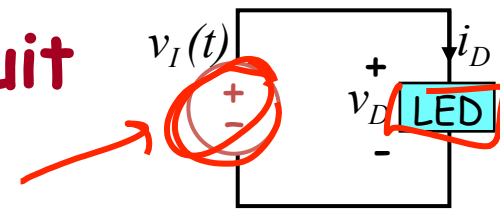For small signals, device behaves like a resistor!




$$I_D = a e^{bV_D}$$

$$I_D = a e^{bV_D}$$

$$i_d = I_D \cdot b \cdot v_d$$

$$i_d = \frac{v_i}{R} = v_i \cdot I_D b$$

We can build a small signal circuit:

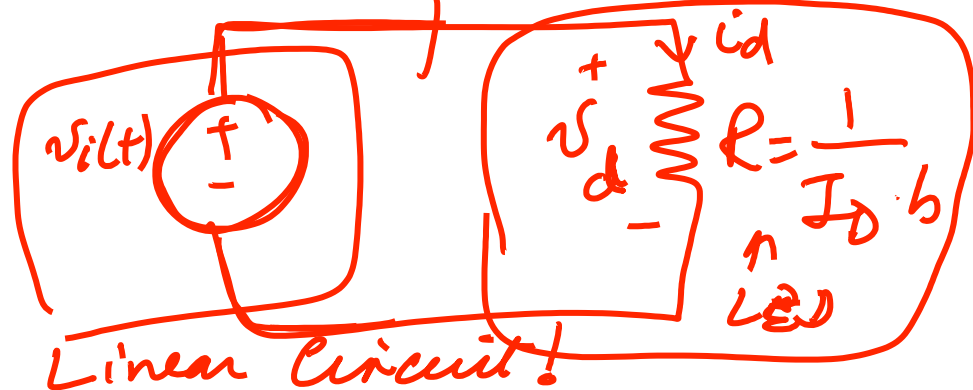

Linear Circuit!

# Small Signal Circuit Method



- Find operating point using DC bias inputs from large signal circuit

*typically involves a nonlinear analysis*

- Develop small signal (linearized) models for each of the elements around the operating point.

*incremental*

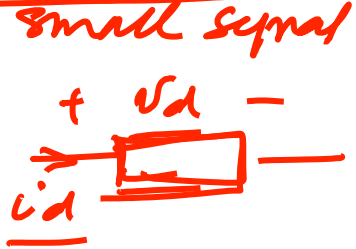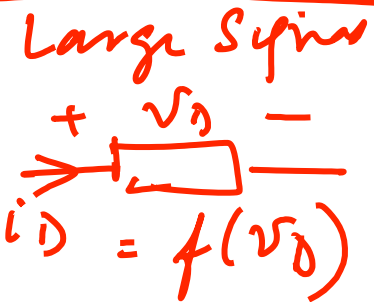*Key: we can use superposition and other linear circuit tools with linearized circuit!*



$i_d = \frac{\partial f(v_D)}{\partial v_D} \cdot v_d$

Replace original elements with small signal element models.


- Analyze resulting linearized circuit to obtain small signal response...

*superposition, Thevenin etc apply*

$i_d = \frac{\partial f(v_D)}{\partial v_D} \bigg|_{v_D = V_D} \cdot v_d$

# Step 2: Voltage Sources and DC Supply $V_0$

large  
signal

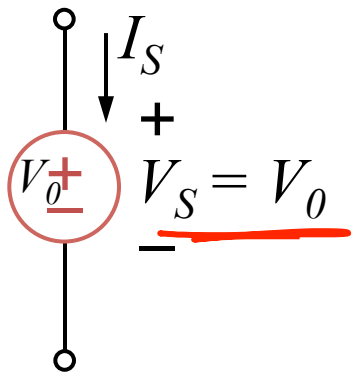

Small  
signal




$$v_1 = \left. \frac{\partial V_0}{\partial i_S} \right|_{i_S = I_S} \cdot i_S$$

$$v_1 = 0$$

$$V_S = V_0$$

$$V_S = f(i_D)$$

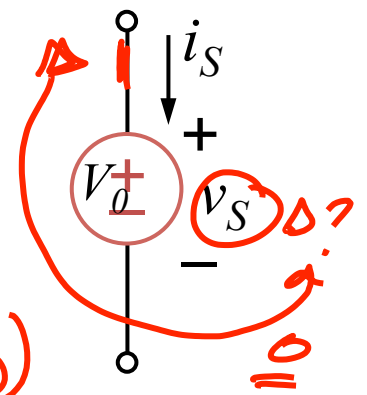


- 1- op pt  $I_{D,Q}$
- 2- lin. modes each side
- 3- analyze lin. det.

DC voltage source behaves as short to small signals.  
DC current source behaves as open to small signals.


See page 416 of textbook

# Current Sources


large  
signal

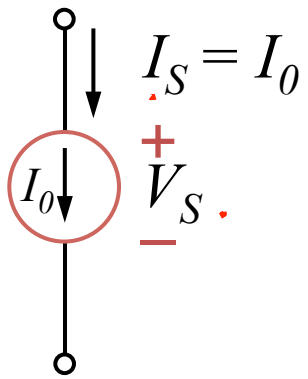

$$I_S = I_0$$

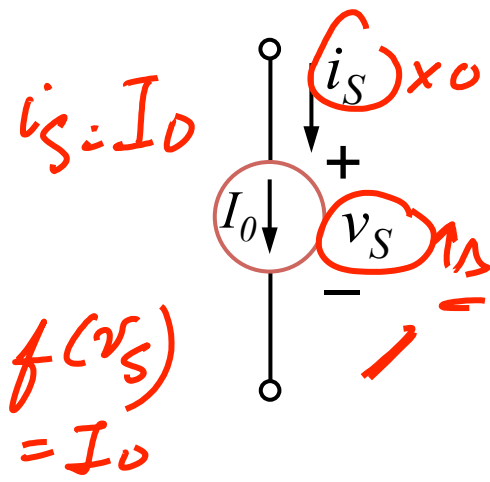

Small  
signal

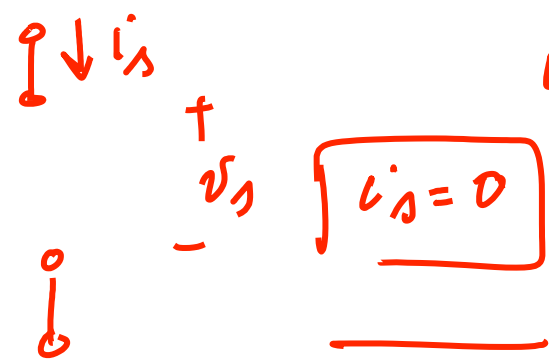


$$i_s = \frac{\partial f(v_s)}{\partial v_s} \bigg|_{v_s = V_S} \cdot v_s$$

$$= \frac{\partial I_0}{\partial v_s} \bigg|_{v_s = V_S} \cdot v_s$$



DC voltage source behaves as short to small signals.  
DC current source behaves as open to small signals.

# Voltage Source Containing Both DC and Small Signal

large  
signal

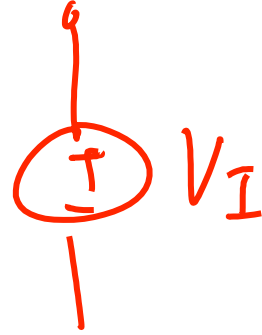


Small  
signal

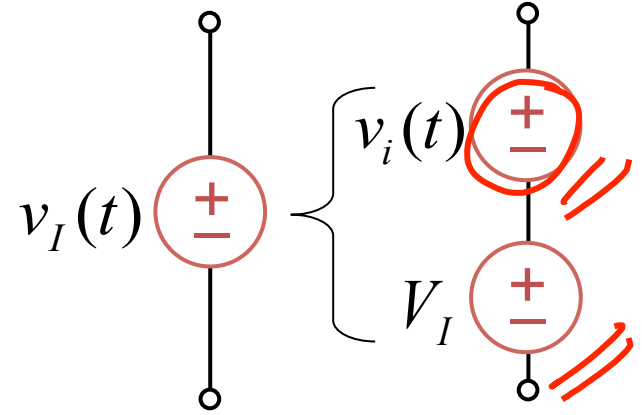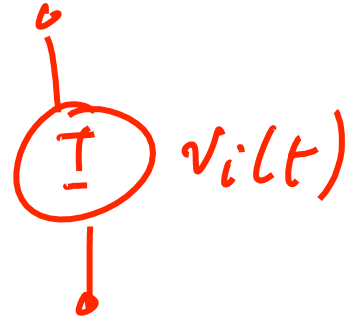


Similarly,  $R$


large  
signal

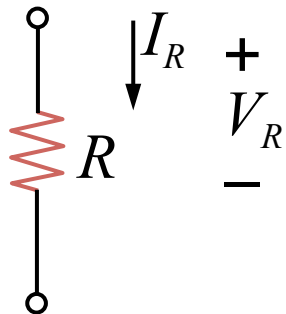

$$V_R = R I_R$$

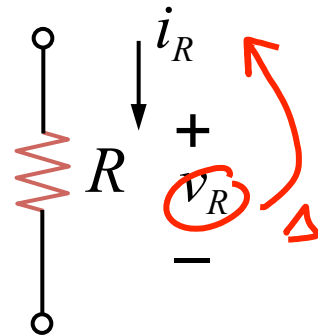

small  
signal

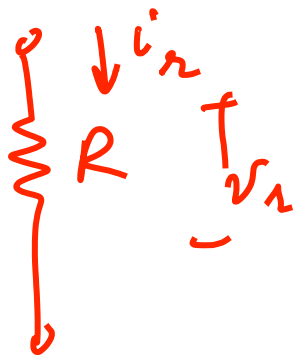

$$v_r = R i_r$$


$$v_r = \frac{\partial (R i_r)}{\partial i_r} \bigg|_{i_r = I_R} \cdot i_r$$

$$\longleftrightarrow v_r = R \cdot i_r$$




# For Non-Linear Device D

large  
signal

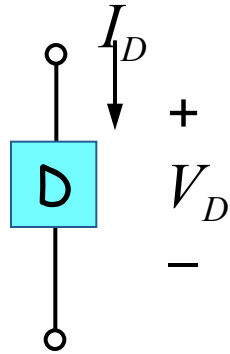

$$I_D = a e^{bV_D}$$

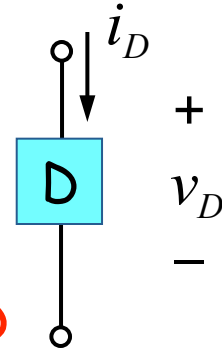

$$i_D = a e^{bv_D}$$

$$i_D = f(v_D)$$

small  
signal



$$i_d = \frac{\partial f(v_D)}{\partial v_D} \bigg|_{v_D = V_D} \cdot v_d$$


$$= a e^{bV_D} = b \bigg|_{v_D = V_D} \cdot v_d$$

$$= a e^{bV_D} \cdot b v_d$$

$$i_d = (I_D b) v_d$$

We will visit small signal circuits again shortly...

# Small signal circuit analysis example

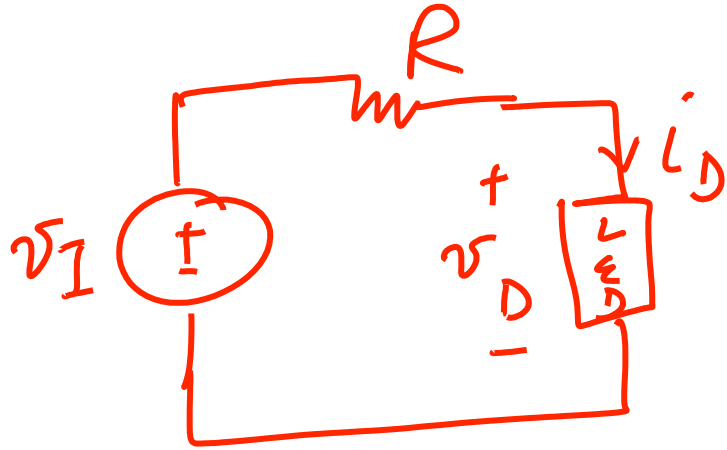

$$i_D = a e^{b V_D}$$

1. large sig analysis
2. linearized model for elements
3. analyze SS ch



Find  $i_D$  for  $V_I$

assume  $R = 1 \Omega$ ,  $a = \frac{1}{4} A$ ,  $b = 1 V^{-1}$

also assume that the bias point set at  $V_I = 1V$

a

# Step 1

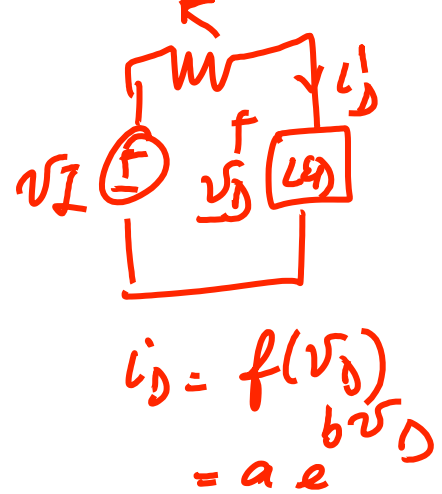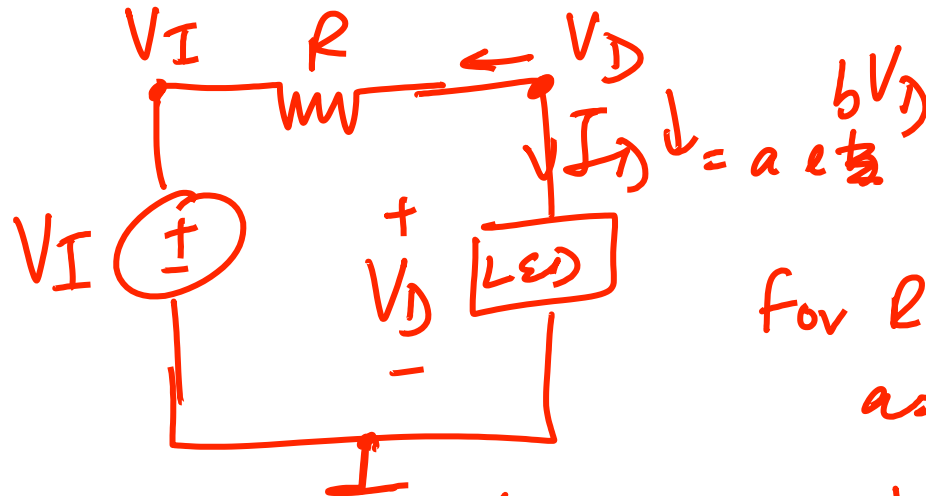

for  $R = 1 \Omega$

$a = \frac{1}{4} A$

$b = \frac{1}{a T - V_I} = 1 V^{-1}$


Analytical method

$\frac{V_D - V_I}{R} + a e^{b V_D} = 0$


$V_D - 1 + \frac{1}{4} e^{V_D} = 0$

$V_D = 0.51 V, I_D = 0.44 A$

# Step 2

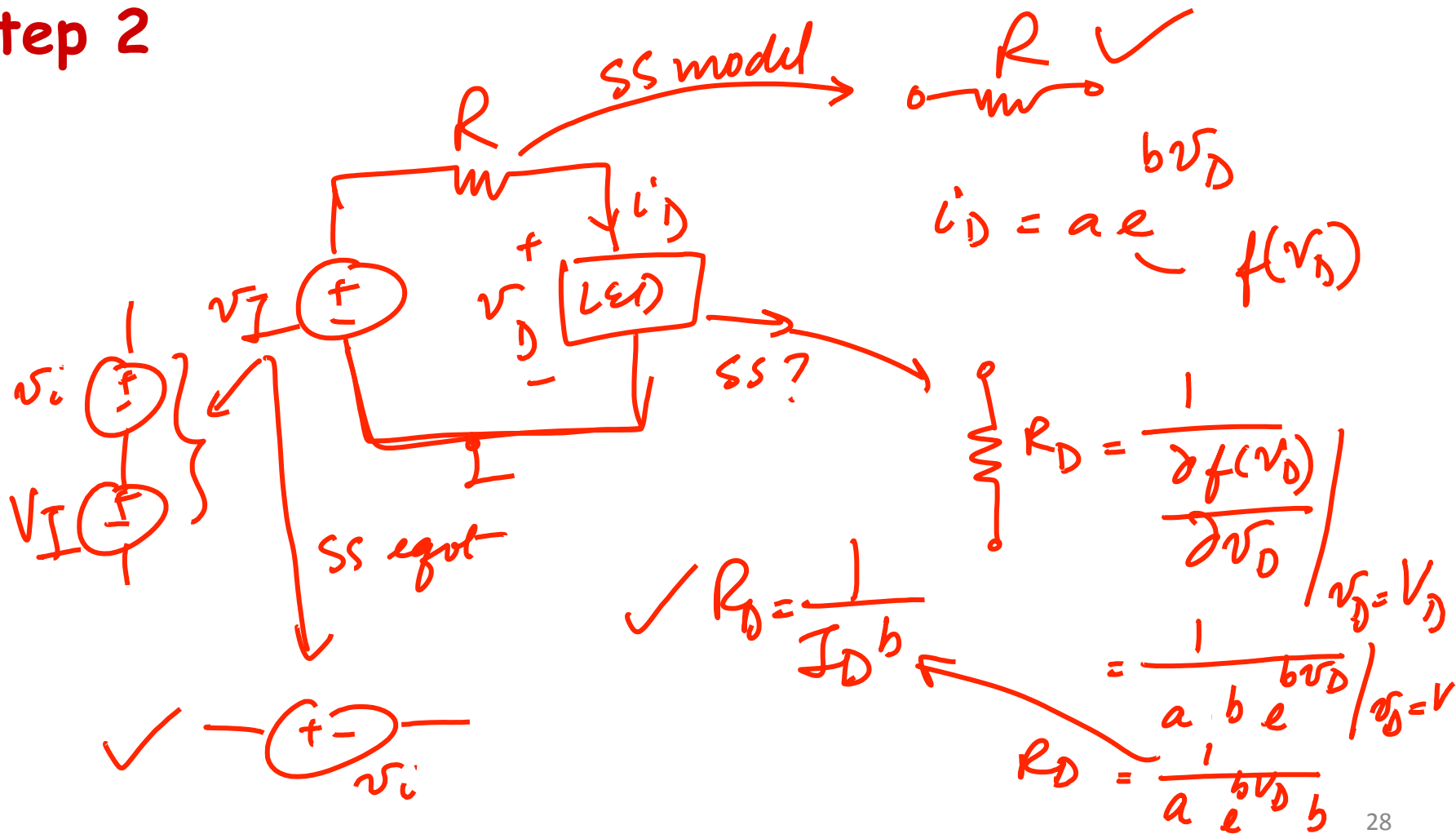

# Step 3

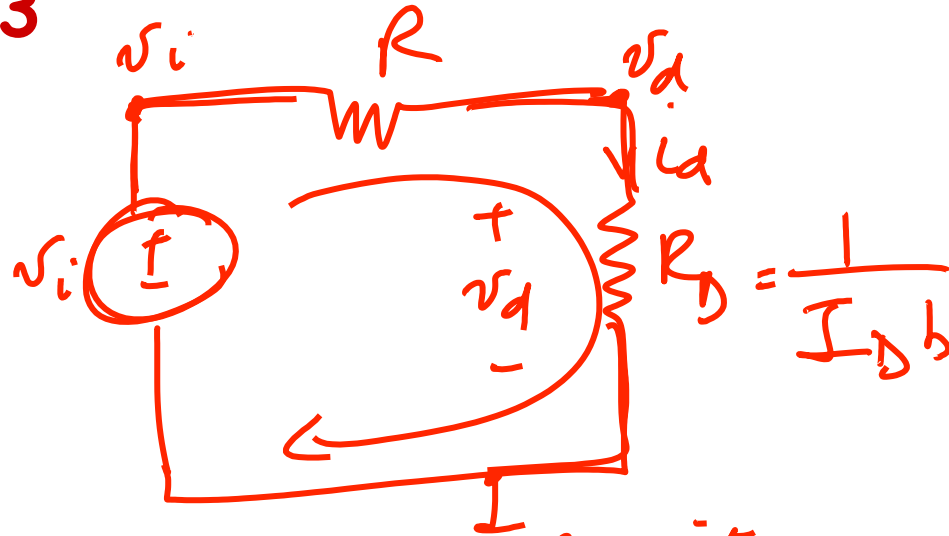

Small Signal Circuit

$i_d$  ?

$$v_d = \frac{v_i}{R + R_D}$$

$$i_d = \frac{1}{\beta} \frac{1}{I_{DQ}}$$

from large signal analysis  
 $I_{DQ} = 0.44 \text{ A}$