


Nature as observed in experiments

...	12	9	6	3	1
	0.4	0.3	0.2	0.1	0


Physics laws or "abstractions"

- Maxwell's
 - Ohm's $V = RI$
- abstraction for tables of data


Lumped circuit abstraction

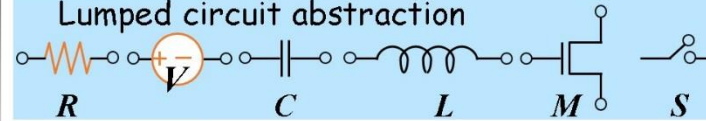


Simple amplifier abstraction

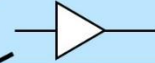

Operational amplifier abstr.

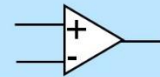


Digital abstraction

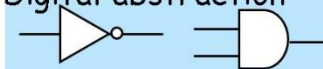

Combinational logic



Filters

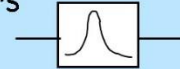

Clocked digital abstraction



Analog subsystems

Modulators,
oscillators,
RF amps,
power supplies 6.061

Instruction set abstraction

Pentium, MIPS 6.004, 6.846

Programming languages

Java, C++, Matlab, Python 6.00

Software systems

Operating systems, Browsers 6.033

Mice, toasters, sonar, stereos, angry birds,
space shuttle, iPad 6.455 6.172, 6.173

6.002x

Lumped Element Abstraction

Consider




The Big Jump
from physics
to EECS

Suppose we wish to answer this question:
What is the current through the bulb?

Reading: Skim through Chapter 1 of A&L

We could do it the Hard Way...

Apply Maxwell's

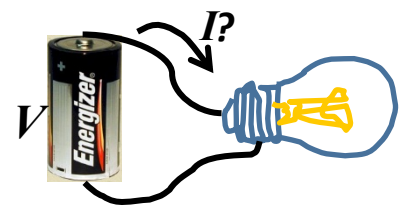

Differential form

Integral form

Faraday's

$$\nabla \times E = -\frac{\partial B}{\partial t}$$

$$\oint E \cdot dl = -\frac{\partial \phi_B}{\partial t}$$

Continuity

$$\nabla \cdot J = -\frac{\partial \rho}{\partial t}$$

$$\oint J \cdot dS = -\frac{\partial q}{\partial t}$$

Others

$$\nabla \cdot E = \frac{\rho}{\epsilon_0}$$

$$\oint E \cdot dS = \frac{q}{\epsilon_0}$$

⋮

⋮

Instead, there is an Easy Way...

First, let us build some insight:

Analogy

I ask you: What is the acceleration?


You quickly ask me: What is the mass?

I tell you:

You respond:

Done!!!

Instead, there is an Easy Way...

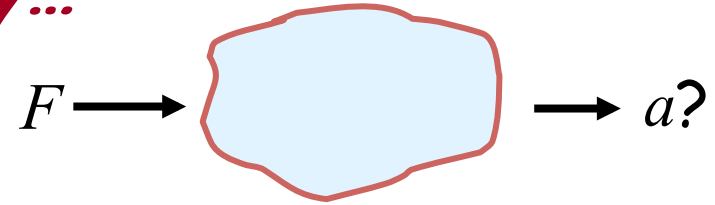


In doing so, you ignored

- the object's shape
- its temperature
- its color
- point of force application
- ...

→ Point-mass discretization

The Easy Way...

Consider the filament of the light bulb.

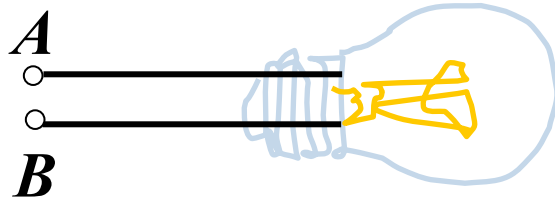

We do not care about

- how current flows inside the filament
- its temperature, shape, orientation, etc.


We can replace the bulb with a

discrete resistor



for the purpose of calculating the current.

The Easy Way...

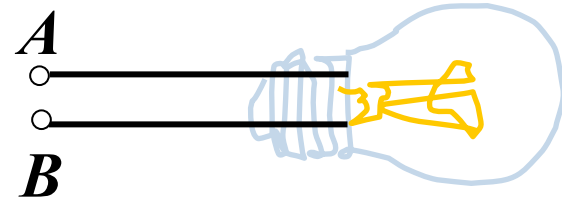Replace the bulb with a
discrete resistor
for the purpose of calculating the current.



The Easy Way...

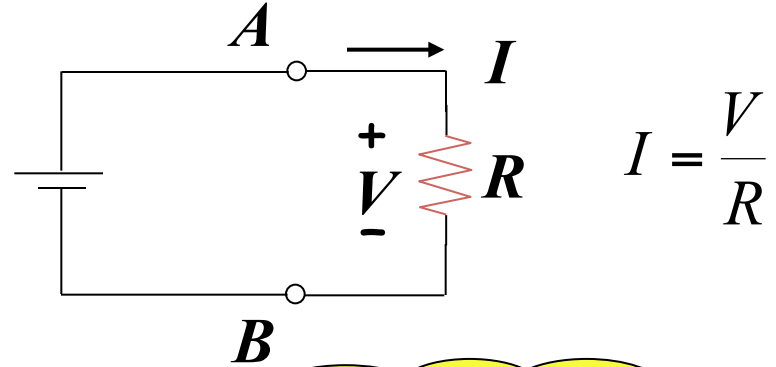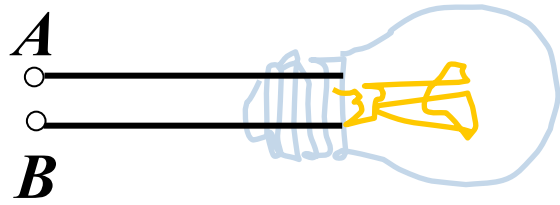


In EECS, we do things
the easy way...

R represents the only property of interest!

Like with point-mass:

replace objects with their mass m to find $a = \frac{F}{m}$

V-I Relationship

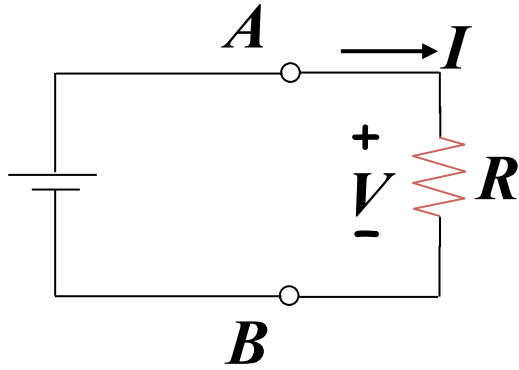

and $I = \frac{V}{R}$

R represents the only property of interest!

R relates element V and I

$I = \frac{V}{R}$ called element v-i relationship



R is a lumped element abstraction for the bulb.

Lumped Elements



Lumped circuit element
described by its vi relation

Power consumed by element = vi

Resistor

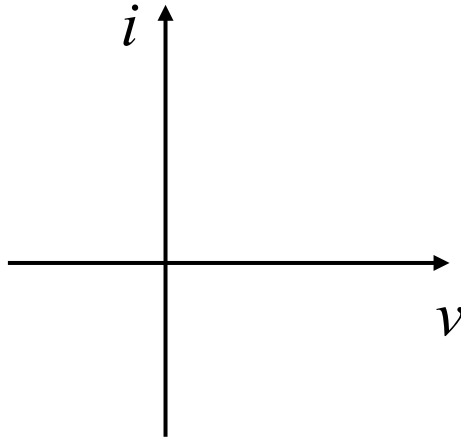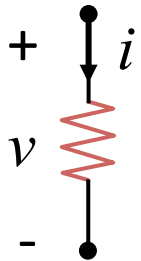

Voltage source

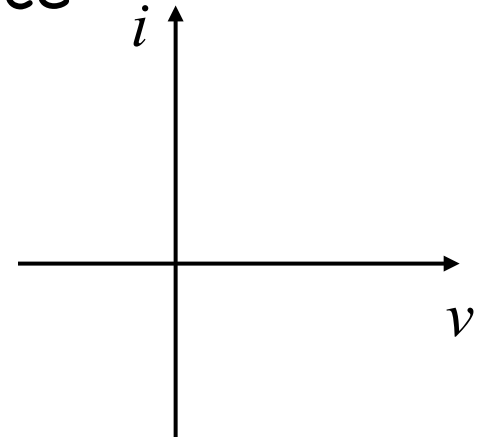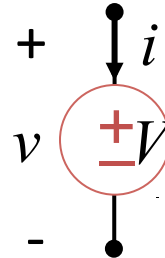


Demo → Lumped element examples
whose behavior is completely
captured by their $V-I$ relationship.

only for the
sorts of
questions we
as EEs would
like to ask!

Demo →
Exploding resistor demo
→ can't predict that!
Pickle demo
→ can't predict light, smell


Not so fast, though ...

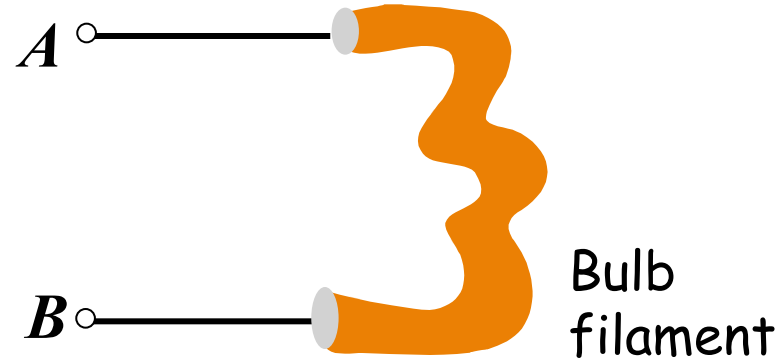

Although we will take the easy way using lumped abstractions for the rest of this course, we must make sure (at least for the first time) that our abstraction is reasonable.

In this case, ensuring that \boxed{V} \boxed{I}
are defined for the element


I must be defined.

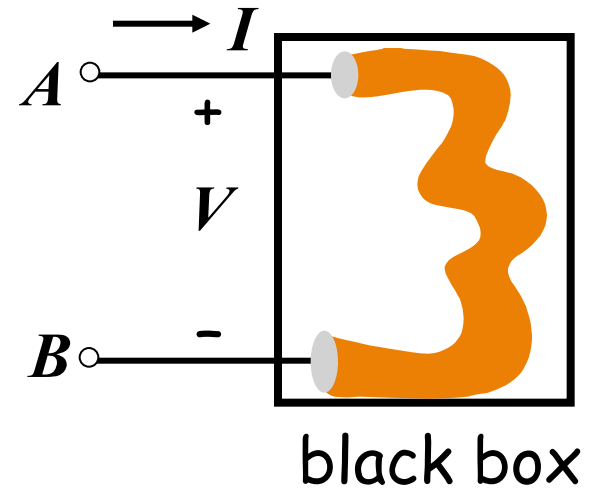

\boxed{I} must be defined. True when

$$I \text{ into } S_A = I \text{ out of } S_B$$

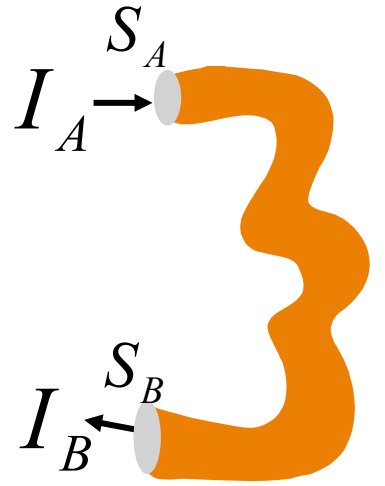True only when $\frac{\partial q}{\partial t} = 0$ in the filament!




$$I_A = I_B \quad \text{only if} \quad \frac{\partial q}{\partial t} = 0$$

So, are we stuck?

We're engineers! So, let's make it true!



Must also be defined.

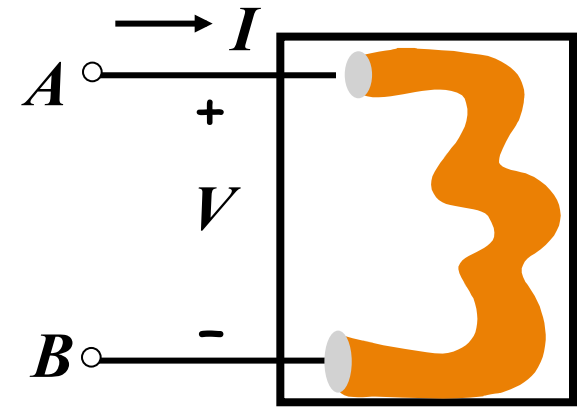

V_{AB} defined when $\frac{\partial \phi_B}{\partial t} = 0$

So $V_{AB} = \int_{AB} E \cdot dl$ outside elements

see
A & L Appendix A.1

So let's assume this too!

Also, signal speeds of interest should be way lower than speed of light

Welcome to the EECS Playground

The world

The EECS playground

Our self imposed constraints in this playground

$\frac{\partial \phi_B}{\partial t} = 0$ Outside


$\frac{\partial q}{\partial t} = 0$ Inside elements
Bulb, wire, battery

Where
good
things
happen



Lumped Matter Discipline (LMD)

Or self imposed constraints:

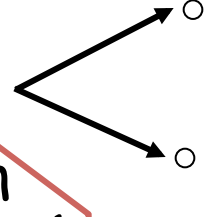

- $\frac{\partial \phi_B}{\partial t} = 0$ outside
- $\frac{\partial q}{\partial t} = 0$ inside elements
bulb, wire, battery


More in
Chapter 1
of A & L

Connecting using ideal wires lumped elements that obey LMD to form an assembly results in the **lumped circuit abstraction**

So, what does LMD buy us?

Replace the differential equations with simple algebra using lumped circuit abstraction (LCA).


For example:

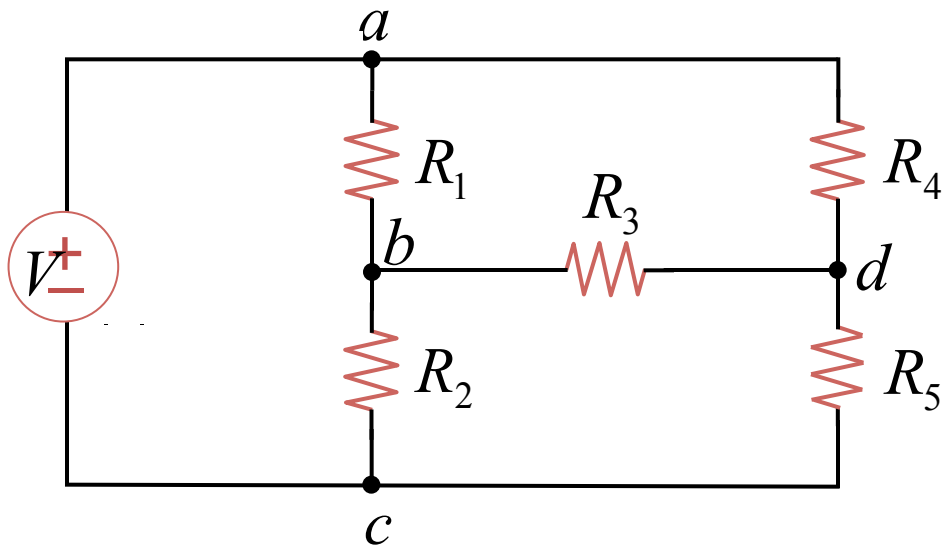

What can we say about voltages in a loop under the lumped matter discipline?

Reading: Chapter 2.1 - 2.2.2 of A&L

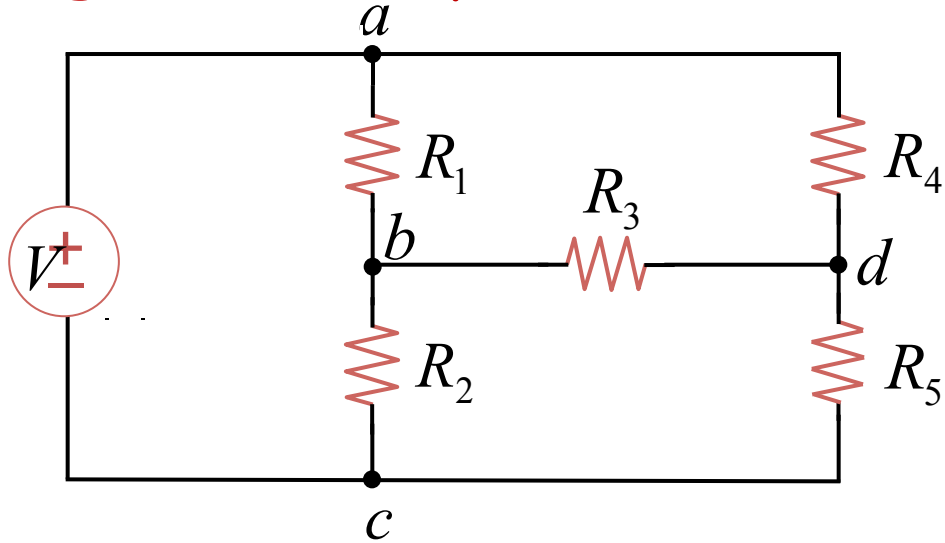
What can we say about voltages in a loop under LMD?




Kirchhoff's Voltage Law (KVL):
The sum of the voltages in a loop is 0.

Remember, this is not true everywhere, only in our EECS playground

What can we say about currents?

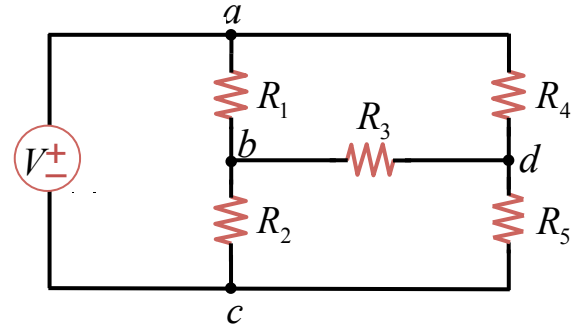

What can we say about currents?

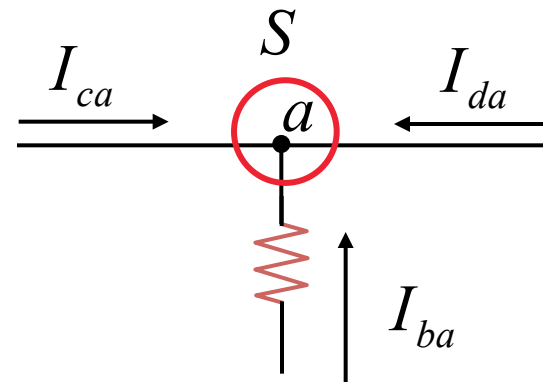

Kirchhoff's Current Law (KCL):

The sum of the currents into a node is 0.

simply conservation of charge

KVL and KCL Summary

KVL:

KCL:

Summary

Lumped Matter Discipline LMD:
Constraints we impose on ourselves to simplify our analysis

$$\frac{\partial \phi_B}{\partial t} = 0$$

Outside elements

$$\frac{\partial q}{\partial t} = 0$$

Inside elements


↓ ↓ ↓
wires resistors sources

Also, signals speeds of interest should be way lower than speed of light

Allows us to create the lumped circuit abstraction

Remember, our EECS playground

Summary

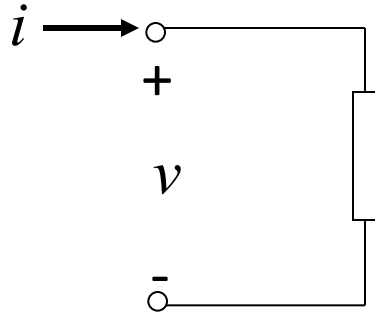

Lumped circuit element

power consumed by element = vi

Summary

Maxwell's equations simplify to algebraic KVL and KCL under LMD.

KVL:

$$\sum_{\text{loop}} v_j = 0$$

This is amazing!

KCL:

$$\sum_j i_j = 0$$

node