

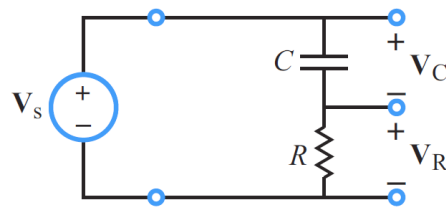



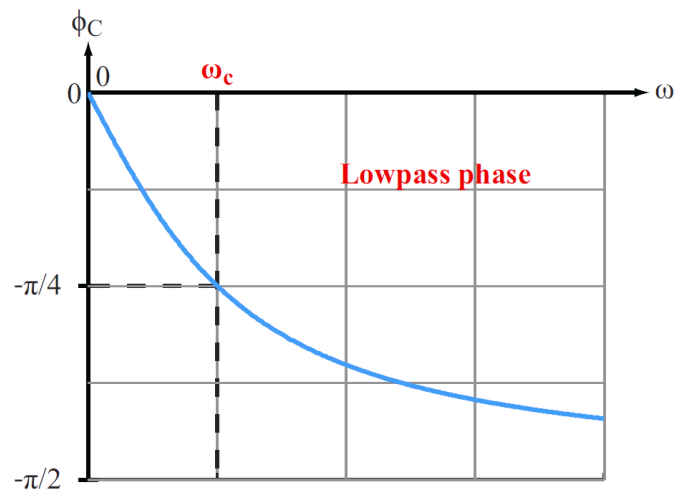
1st order Low and High Pass RC Filter Example



(a) RC circuit

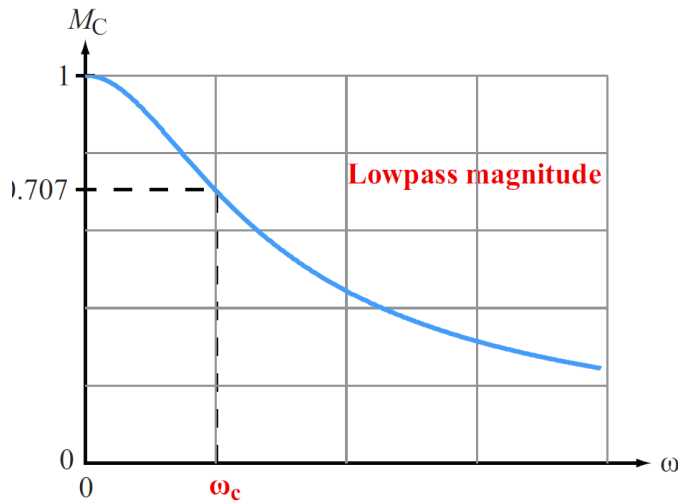

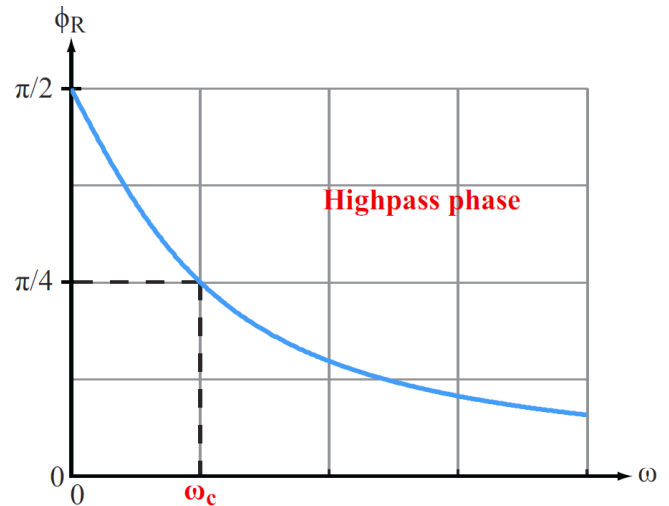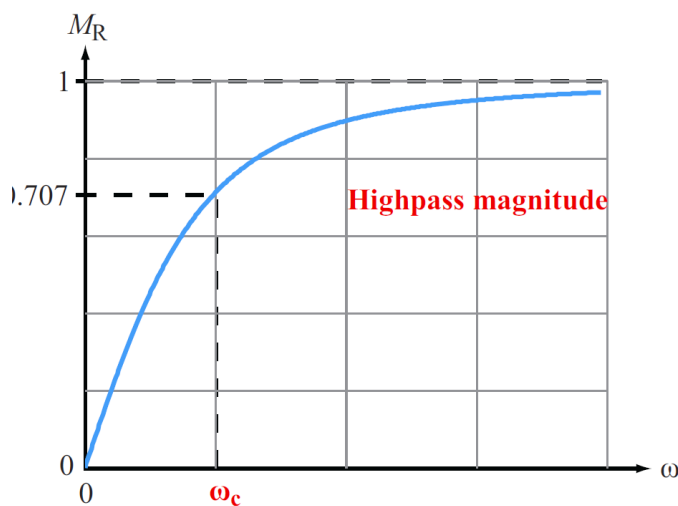(b) Magnitude and phase angle of $\hat{H}_C(\omega) = V_C / V_s$



(c) Magnitude and phase angle of $\hat{H}_R(\omega) = V_R / V_s$

(a) An RC circuit; (b) if we measure the voltage across the capacitor (given the input V_s), we obtain a lowpass filter; (c) if we measure the voltage across the resistor (given the input V_s), we obtain a highpass filter. The expressions that generate the plots above are worked out on the next page.

The Lowpass Filter

Application of voltage division gives

$$\mathbf{V}_C = \frac{\mathbf{V}_s \mathbf{Z}_C}{R + \mathbf{Z}_C} = \frac{\mathbf{V}_s / j\omega C}{R + \frac{1}{j\omega C}}.$$

The transfer function corresponding to \mathbf{V}_C is

$$\mathbf{H}_C(\omega) = \frac{\mathbf{V}_C}{\mathbf{V}_s} = \frac{1}{1 + j\omega RC},$$

where we have multiplied the numerator and denominator of the top expression by $j\omega C$ to simplify the form of the expression. In terms of its magnitude $M_C(\omega)$ and phase angle $\phi_C(\omega)$, the transfer function is given by

$$\mathbf{H}_C(\omega) = M_C(\omega) e^{j\phi_C(\omega)},$$

with

$$M_C(\omega) = |\mathbf{H}_C(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

and

$$\phi_C(\omega) = -\tan^{-1}(\omega RC).$$

At dc, the capacitor acts like an open circuit—allowing no current to flow through the loop—with the obvious consequence that $\mathbf{V}_C = \mathbf{V}_s$. At very high values of ω , the capacitor acts like a short circuit, in which case the voltage across it is approximately zero.

The Highpass Filter

The output across R is

$$\mathbf{H}_R(\omega) = \frac{\mathbf{V}_R}{\mathbf{V}_s} = \frac{j\omega RC}{1 + j\omega RC}$$

The magnitude and phase angle of $\mathbf{H}_R(\omega)$ are given by

$$M_R(\omega) = |\mathbf{H}_R(\omega)| = \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}}$$

And

$$\phi_R(\omega) = \frac{\pi}{2} - \tan^{-1}(\omega RC)$$