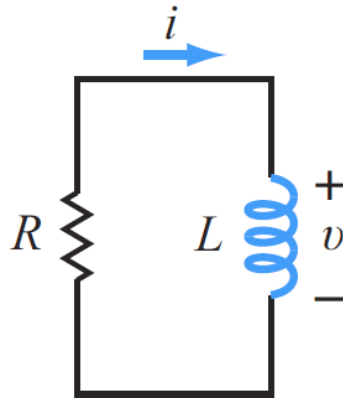


Natural Response of an RL Circuit

Consider the circuit below. Assume we know that the inductor, L , has an initial current $i(0)$ through it. What is the current, i , through L , for $t \geq 0$?



Applying KVL, we can write:

$$Ri + L \frac{di}{dt} = 0$$

We can clean this up a bit by dividing by L :

$$\frac{di}{dt} + ai = 0$$

Where:

$$a = \frac{R}{L}$$

This is a differential equation. Just as in the RC case, it turns out the solution to the differential equation in the blue box above is:

$$i(t) = i(0) e^{-t/\tau} \quad (\text{for } t \geq 0),$$

where:

$$\tau = \frac{1}{a} = \frac{L}{R}.$$

Once we know the current, i , we can also determine:

- the voltage across the inductor, v (since $v = L \cdot di/dt$ for an inductor)
- the power being absorbed or injected by the inductor (since $P = i \cdot v$)
- the energy stored in the inductor at any time (since $U = \int P$ or $\frac{1}{2} \cdot Li^2$)

What does the *time constant*, τ , tell us?

Just as with the RC circuit, the magnitude of the time constant τ is a measure of how fast or how slowly a circuit responds to a sudden change.

- Notice that the units of τ are seconds (that is henrys / ohms = seconds).
- After 1τ , the capacitor has discharged to 0.37 of the initial value.
- After about 5τ , $v(t)$ has dropped to <1% of its original value. Engineers assume 5τ is long enough for particular RL circuit to charge or discharge to its final value.