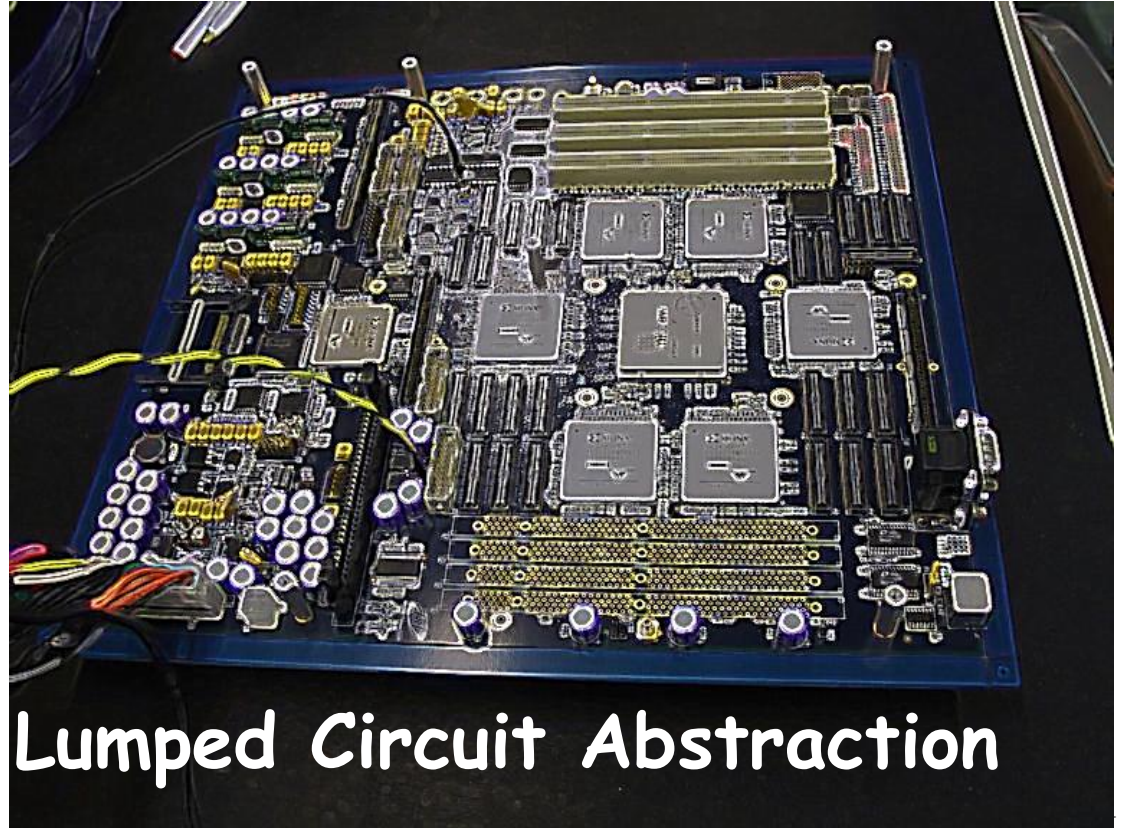


6.002x


# CIRCUITS AND ELECTRONICS



Introduction and Lumped Circuit Abstraction



...and this

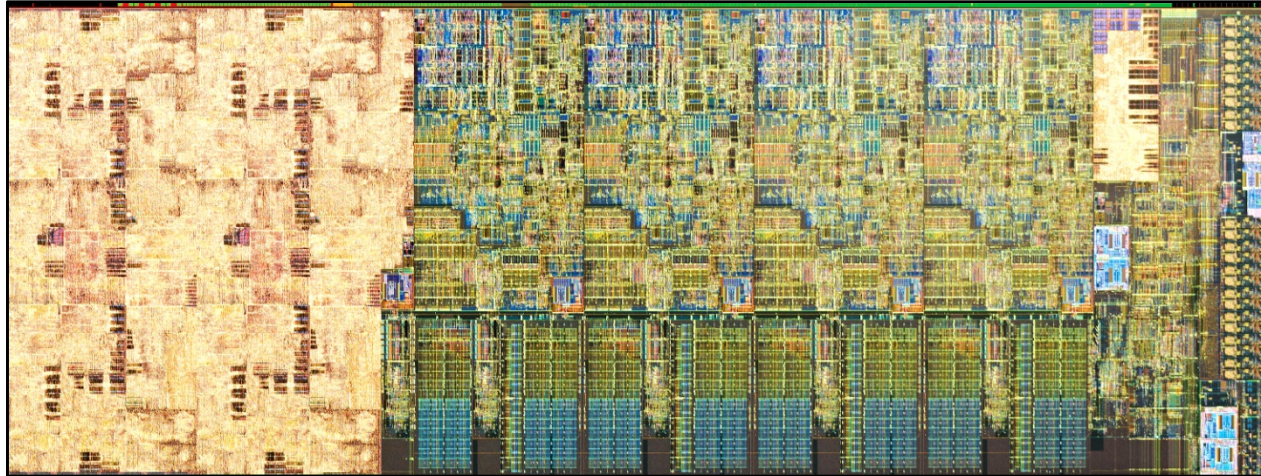

Chip photo of Intel's 22nm multicore processor codenamed Ivy Bridge

Photograph courtesy of Intel Corp.

# ADMINISTRIVIA

## ■ Prerequisites

- AP level course on electricity and magnetism; e.g., MIT's 8.02 (check it out on MIT OpenCourseware)

- It is also useful to have a basic knowledge of solving simple differential equations

## ■ Textbook Agarwal and Lang (A&L)

Underlined readings (in course-at-a-glance handout) are very important as they stress intuition

- Weekly homeworks and labs must be completed by the deadline indicated on the assignment

## ■ Assessments

Homeworks 15%

Labs 15%

1 Midterm 30%

Final exam 40%

## What is engineering?

Purposeful use of science

## What is 6.002x about?

Gainful employment of Maxwell's equations  
From electrons to digital gates and op-amps




Nature as observed in experiments

-	...	4	3	2	1
		0.4	0.3	0.2	0.1

Physics laws or "abstractions"

- Maxwell's abstraction for tables of data
- Ohm's  $V = RI$


Lumped circuit abstraction

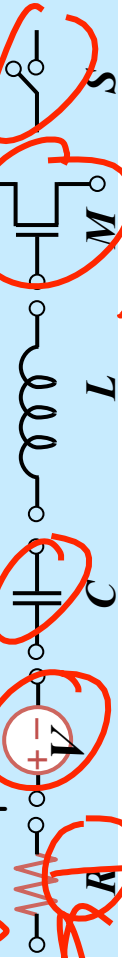

Simple amplifier abstraction



Operational amplifier abstr.

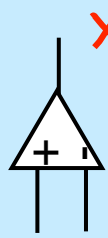

Filters



Analog subsystems

- Modulators, oscillators, RF amps, power supplies

Mice, toasters, sonar, stereos, angry birds, space shuttle, iPad


Digital abstraction



Combinational logic



Clocked digital abstraction

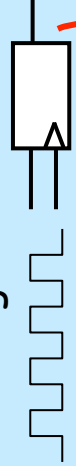

Instruction set abstraction

Pentium, MIPS ISA, 6.004, 6.846

Programming languages

Java, C++, Matlab, Python


Software systems systems, Browsers

Operating systems

6.002x

# Lumped Element Abstraction

Consider

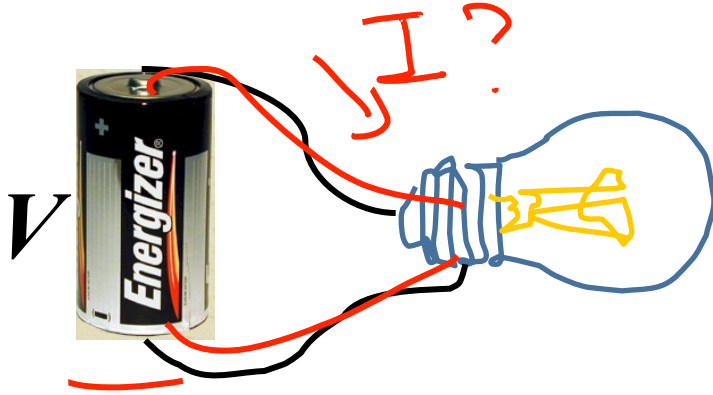


The Big Jump  
from physics  
to EECS

Suppose we wish to answer this question:  
What is the current through the bulb?

Reading: Skim through Chapter 1 of A&L

*We could do it the Hard Way...*

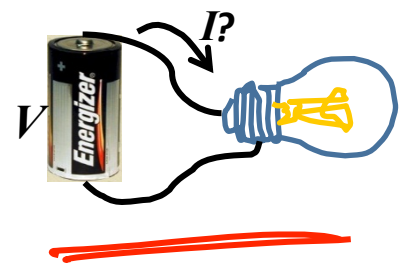

Apply Maxwell's

Differential form

Integral form

Faraday's

$$\nabla \times E = -\frac{\partial B}{\partial t}$$

$$\oint E \cdot dl = -\frac{\partial \phi_B}{\partial t}$$

Continuity

$$\nabla \cdot J = -\frac{\partial \rho}{\partial t}$$

$$\oint J \cdot dS = -\frac{\partial q}{\partial t}$$

Others

$$\nabla \cdot E = \frac{\rho}{\epsilon_0}$$

$$\oint E \cdot dS = \frac{q}{\epsilon_0}$$

⋮


⋮



# Instead, there is an Easy Way...

First, let us build some insight:

Analogy

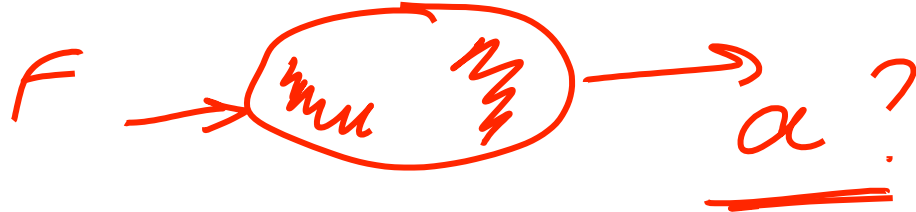

I ask you: What is the acceleration?

You quickly ask me: What is the mass?  $m$


I tell you:  $m$

You respond:

$$a = \frac{F}{m}$$

Done!!!

# *Instead, there is an Easy Way...*

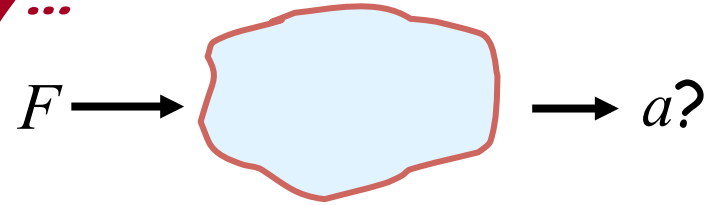

In doing so, you ignored



- the object's shape
- its temperature
- its color
- point of force application
- ...

$m$   
=

→ Point-mass discretization

# The Easy Way...

Consider the filament of the light bulb.

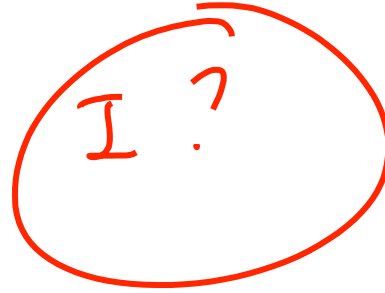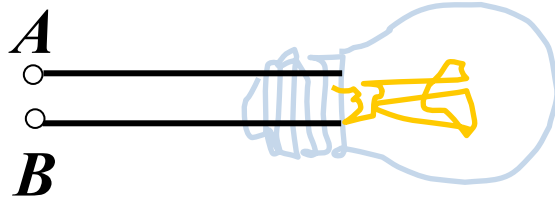

We do not care about

- how current flows inside the filament
- its temperature, shape, orientation, etc.



We can replace the bulb with a

*discrete resistor*

for the purpose of calculating the current.

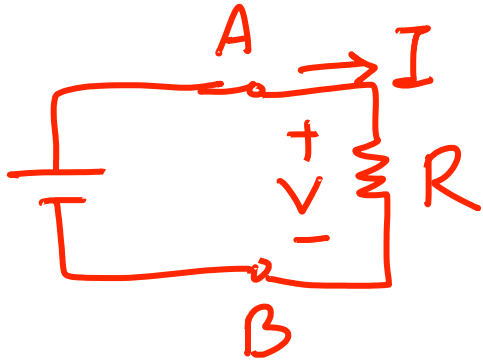
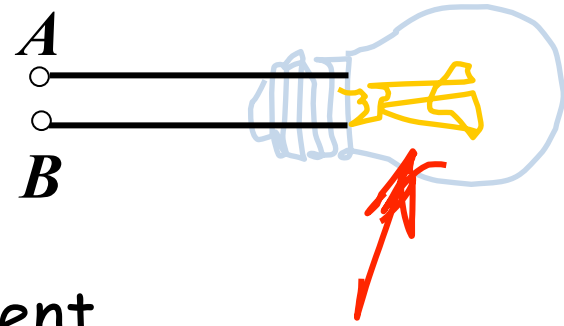
# The Easy Way...

Replace the bulb with a  
*discrete resistor*  
for the purpose of calculating the current.



$$I = \frac{V}{R}$$

# The Easy Way...

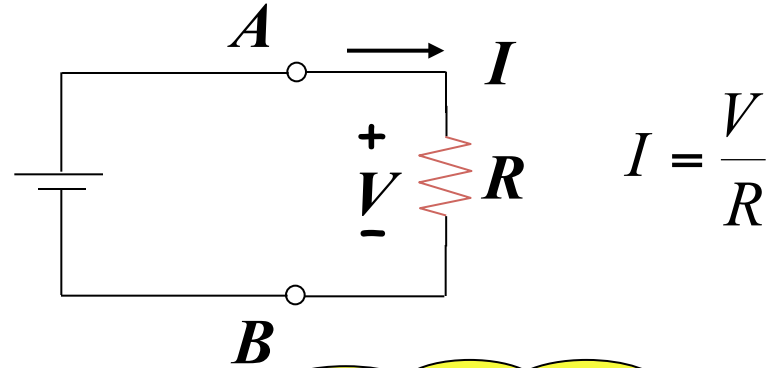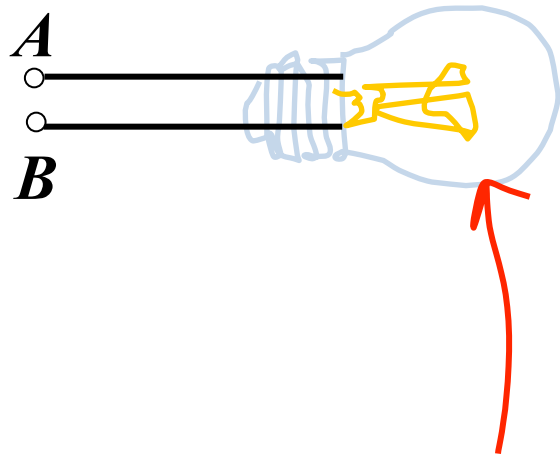

In EECS, we do things the easy way...


*R* represents the only property of interest!

Like with point-mass:

replace objects with their mass *m* to find

$$a = \frac{F}{m}$$

# V-I Relationship

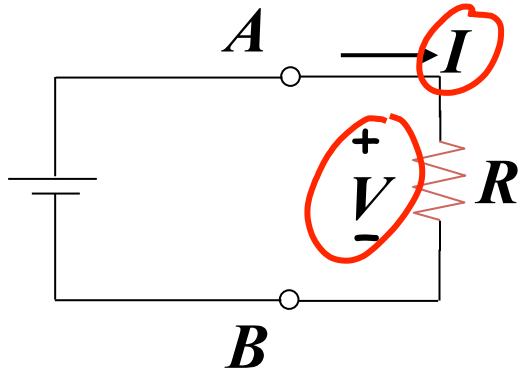

and  $I = \frac{V}{R}$

$R$  represents the only property of interest!


$R$  relates element  $V$  and  $I$

$$I = \frac{V}{R}$$

Red handwritten equation with an arrow pointing from the 'I' in the equation to the 'I' in the text above.

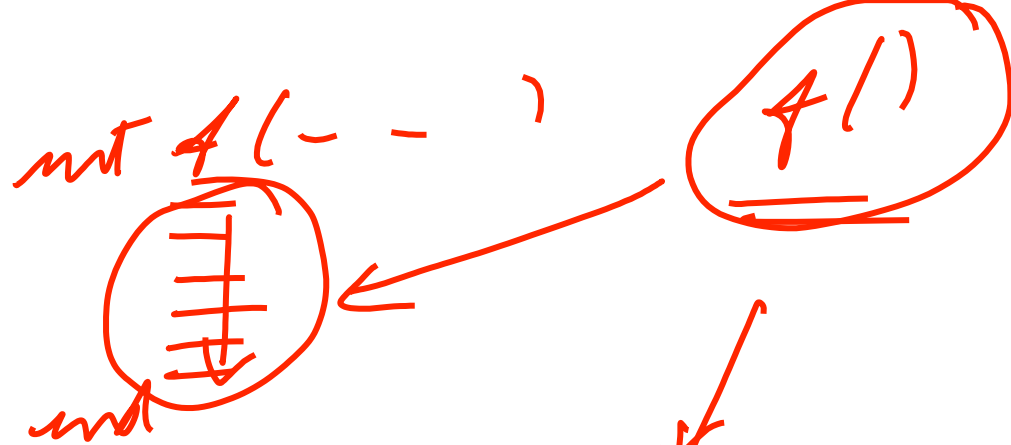$I = \frac{V}{R}$  called element v-i relationship






---

$R$  is a lumped element abstraction for the bulb.

---





# Lumped Elements

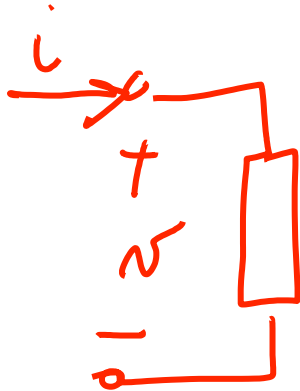



Lumped circuit element described by its  $vi$  relation

Power consumed by element =  $vi$

Resistor

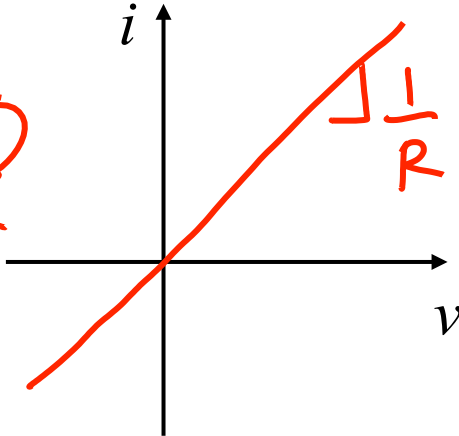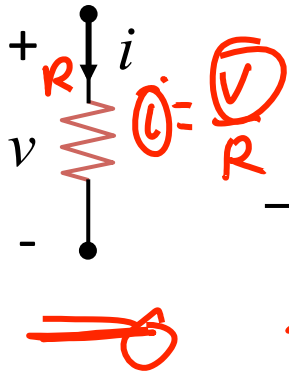

Voltage source

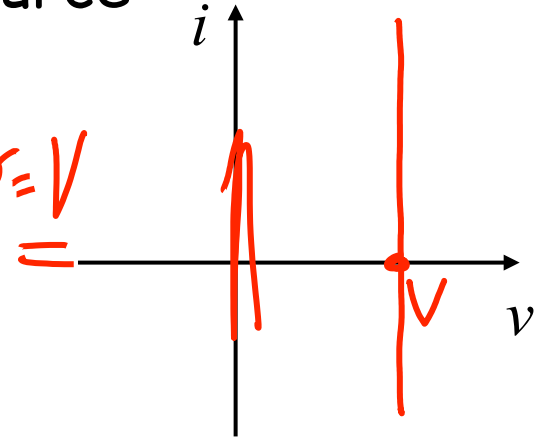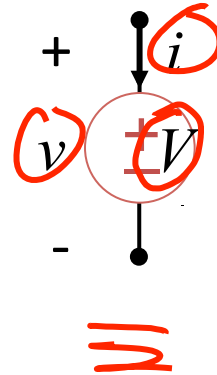


**Demo** → Lumped element examples  
whose behavior is completely  
captured by their  $V-I$  relationship.

only for the  
sorts of  
questions we  
as EEs would  
like to ask!

**Demo** →  
Exploding resistor demo  
→ can't predict that!  
Pickle demo  
→ can't predict light, smell

Not so fast, though ...

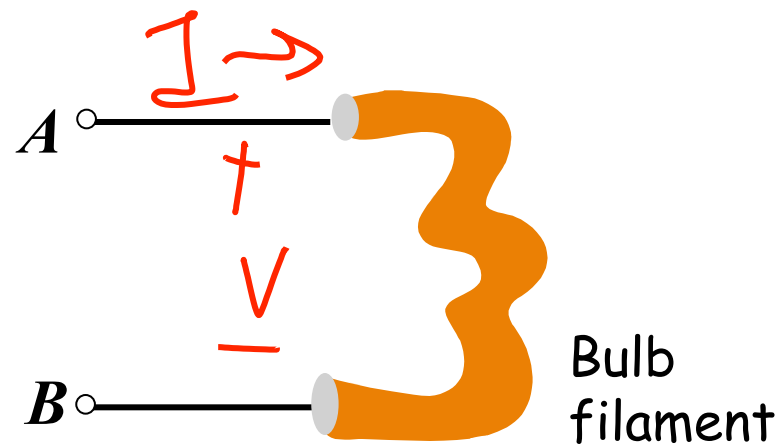


Although we will take the easy way using lumped abstractions for the rest of this course, we must make sure (at least for the first time) that our abstraction is reasonable.

In this case, ensuring that  $V$   $I$  are defined for the element

$I$  must be defined.
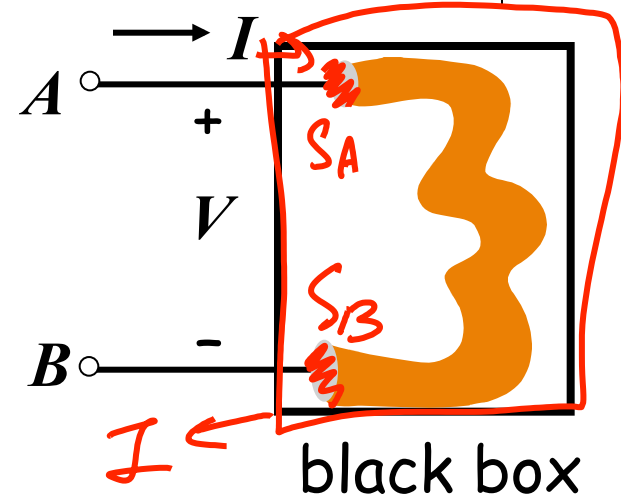
$$I \text{ into } S_A = I \text{ out of } S_B$$



**I** must be defined. True when

$$I \text{ into } S_A = I \text{ out of } S_B$$



True only when  $\frac{\partial q}{\partial t} = 0$  in the filament!

from Maxwell

$$\int_{S_A} \mathbf{J} \cdot d\mathbf{S} - \int_{S_B} \mathbf{J} \cdot d\mathbf{S} = \frac{\partial q}{\partial t}$$

$I_A$                        $I_B$

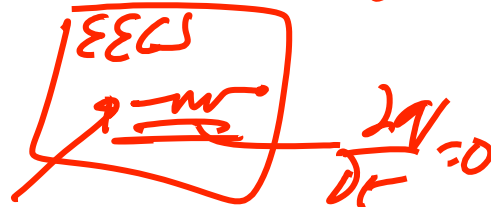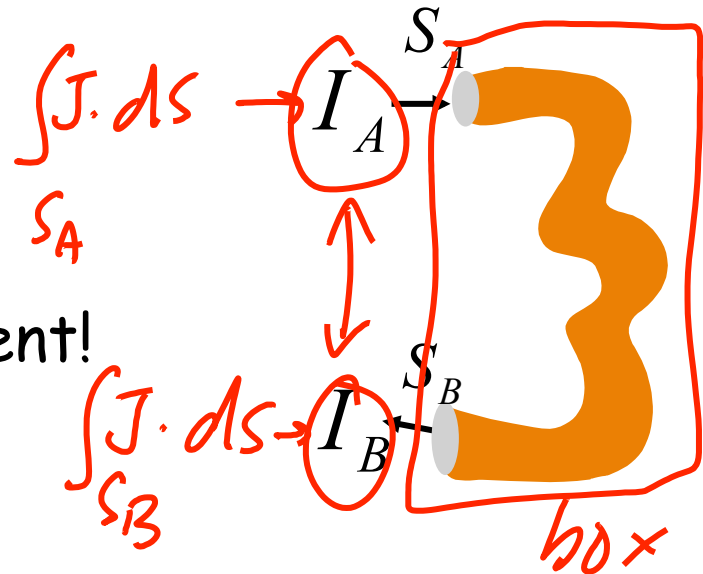$I_A = I_B$  only if  $\frac{\partial q}{\partial t} = 0$




So, are we stuck?

**We're engineers! So, let's make it true!**



$V$  Must also be defined.

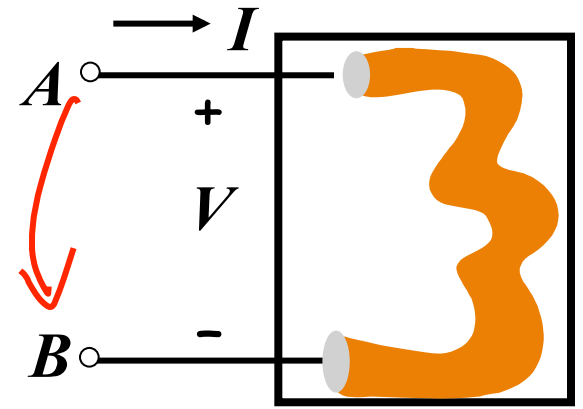

$V_{AB}$  defined  $\frac{\partial \phi_B}{\partial t}$

$V_{AB}$  defined when  $\frac{\partial \phi_B}{\partial t} = 0$

So  $V_{AB} = \int_{AB} E \cdot dl$  outside elements

see A & L Appendix A.3

So let's assume this too

①  $\frac{\partial \phi}{\partial t} = 0$

②  $\frac{\partial \phi_B}{\partial t} = 0$


Also, signal speeds of interest should be way lower than speed of light

# Welcome to the EECS Playground

The world
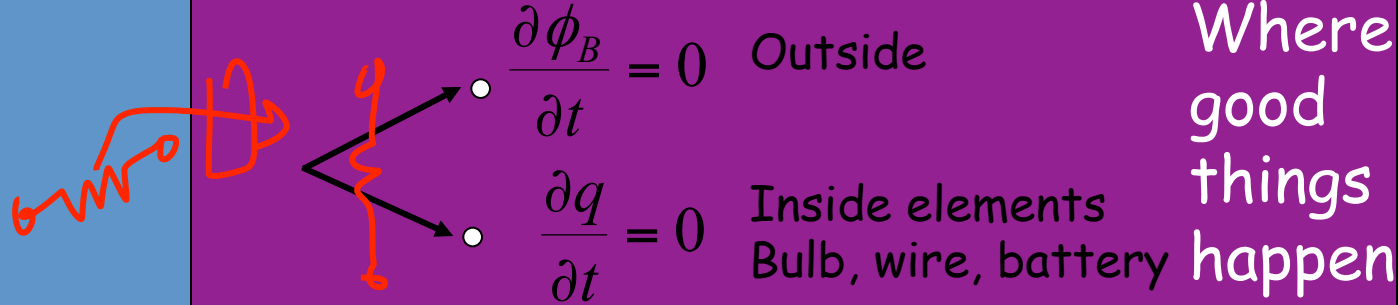
## The EECS playground

Our self imposed constraints in this playground




# Lumped Matter Discipline (LMD)

Or self imposed constraints:

- $\frac{\partial \phi_B}{\partial t} = 0$  outside
- $\frac{\partial q}{\partial t} = 0$  inside elements  
bulb, wire, battery

More in  
Chapter 1  
of A & L

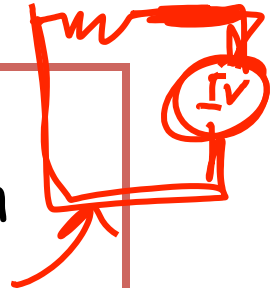Connecting using ideal wires lumped elements that obey LMD to form an assembly results in the **lumped circuit abstraction**




# So, what does LMD buy us?

Replace the differential equations with simple algebra using lumped circuit abstraction (LCA).

$$2a + 3b = 0 \dots$$

For example:

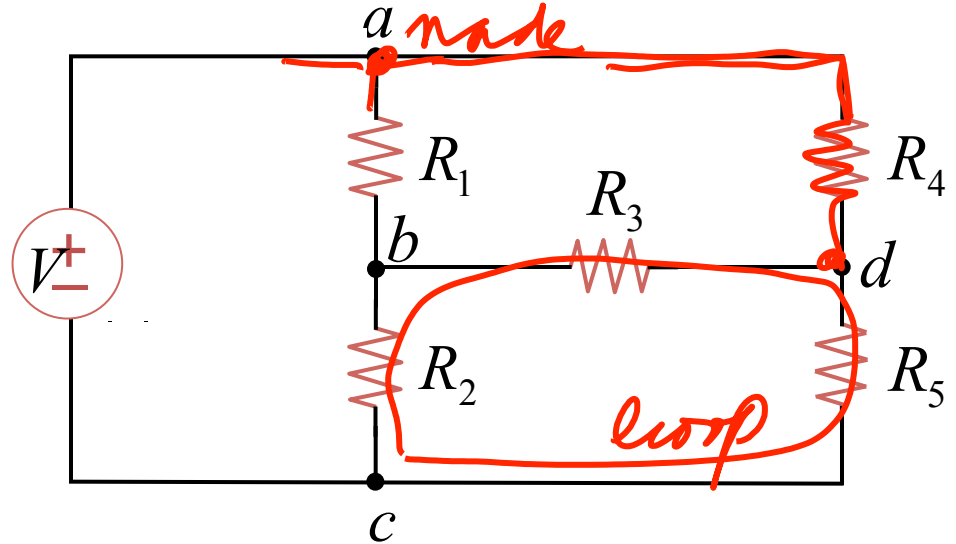

What can we say about voltages in a loop under the lumped matter discipline?

Reading: Chapter 2.1 - 2.2.2 of A&L


What can we say about voltages in a loop under LMD?

$$\oint \mathbf{E} \cdot d\mathbf{l} = \frac{-\partial \Phi_B}{\partial t}$$

LMD  
G

$$\Rightarrow \int_{ca} \mathbf{E} \cdot d\mathbf{l} + \int_{ab} \mathbf{E} \cdot d\mathbf{l} + \int_{bc} \mathbf{E} \cdot d\mathbf{l} = 0$$
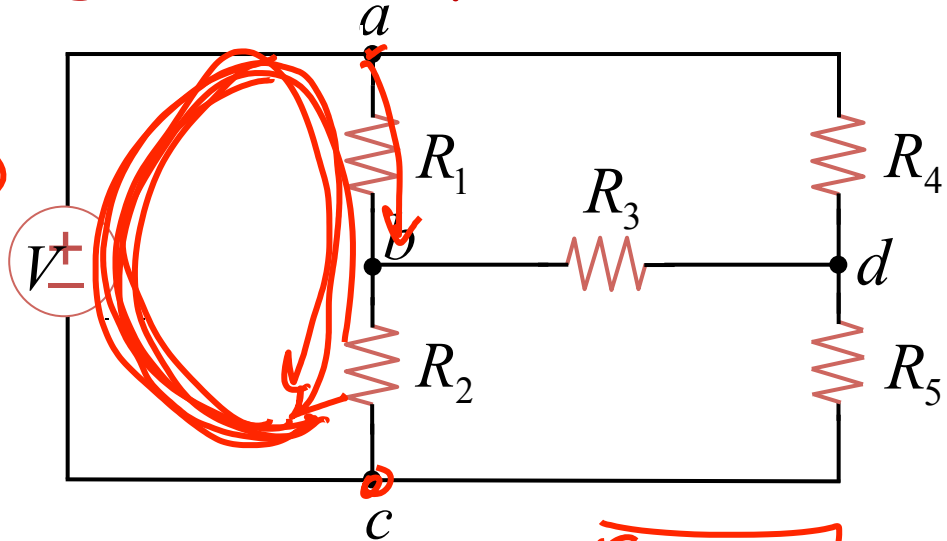
$$\rightarrow V_{ca} + V_{ab} + V_{bc} = 0$$





EECS

Kirchhoff's Voltage Law (KVL):

The sum of the voltages in a loop is 0.

Remember, this is not true everywhere, only in our EECS playground

# What can we say about currents?

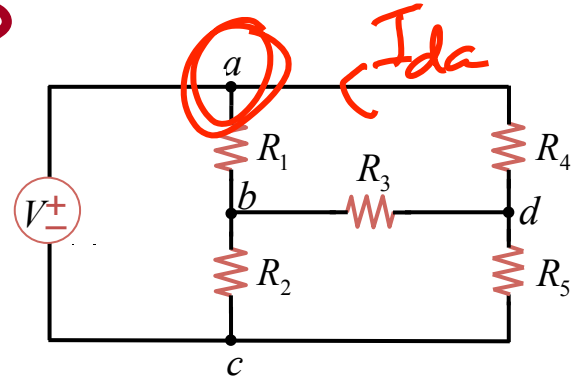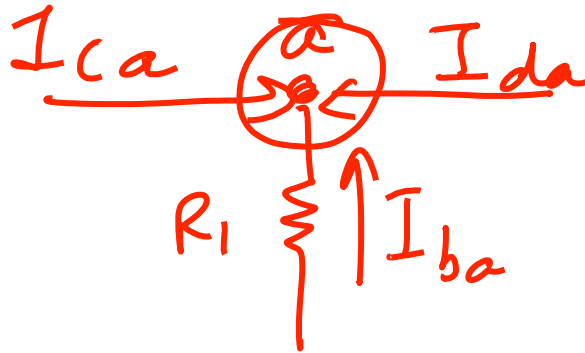



# What can we say about currents?


$$\oint_S \mathbf{J} \cdot d\mathbf{s} = -\frac{\partial q}{\partial t} \rightarrow 0 \text{ M.D. !}$$

$$\Rightarrow I_{ca} + I_{da} + I_{ba} = 0$$

Kirchhoff's Current Law (KCL):

The sum of the currents into a node is 0.

simply conservation of charge

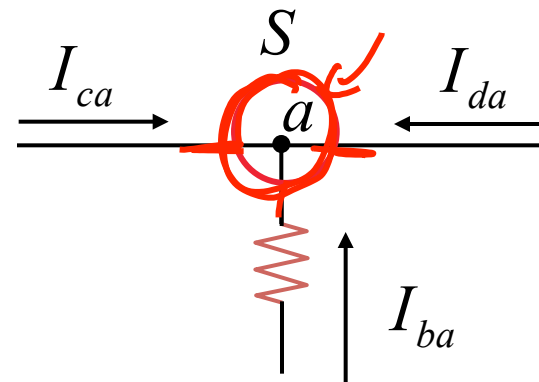

# KVL and KCL Summary

KVL:

$$\sum_{\text{loop}} v_j = 0$$

KCL:

$$\sum_i i_i = 0$$

node

# Summary

Lumped Matter Discipline LMD:  
Constraints we impose on ourselves to simplify our analysis

$$\frac{\partial \phi_B}{\partial t} = 0$$

Outside elements

$$\frac{\partial q}{\partial t} = 0$$

Inside elements

wires resistors sources


Also, signals speeds of interest should be way lower than speed of light

Allows us to create the lumped circuit abstraction

Remember, our EECS playground



# Summary

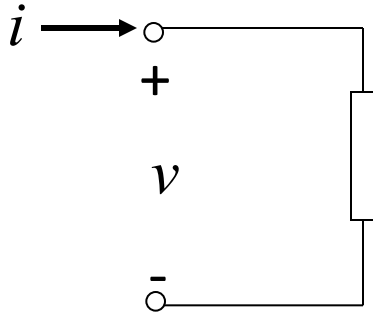

Lumped circuit element

power consumed by element =  $vi$

$$i = f(v)$$
$$i = \frac{v}{R}$$
$$i = 6.7v^2 + \frac{v+1}{2}$$

# Summary

Maxwell's equations simplify to algebraic KVL and KCL under LMD.

KVL:

$$\sum_j v_j = 0$$

loop

This is amazing!

KCL:

$$\sum_j i_j = 0$$

node