6.002x

CIRCUITS AND ELECTRONICS Impulses, Steps and Ramps

#### In our previous sequence...

Slower may be better

### In our previous sequence...

6.002x expert saw Sand - make the translion slower the solution! Somed \_no glithe

We will see why here...

## We will also understand how to model drug delivery




If the input duration is much shorter than system time constant, then shape or duration of input does not matter, only total amount of drug delivered.

Model input as a short pulse → Impulse

## First, let's understand a step input


## Rising step response of RC circuit

## Falling step response of RC circuit

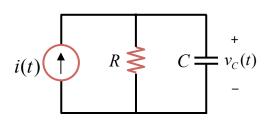

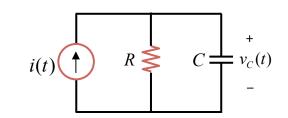
## Pulse input:

Rising step followed by falling step (much later)!


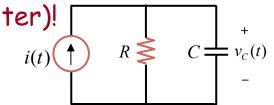
### Short pulse input:


Rising step followed by falling step (shortly thereafter)! [



#### Let's Stare at Current Pulse


Becomes "impulse" as Lim T  $\rightarrow$  0 Denoted by  $\delta(t)$ Impulse is an important signal type 10
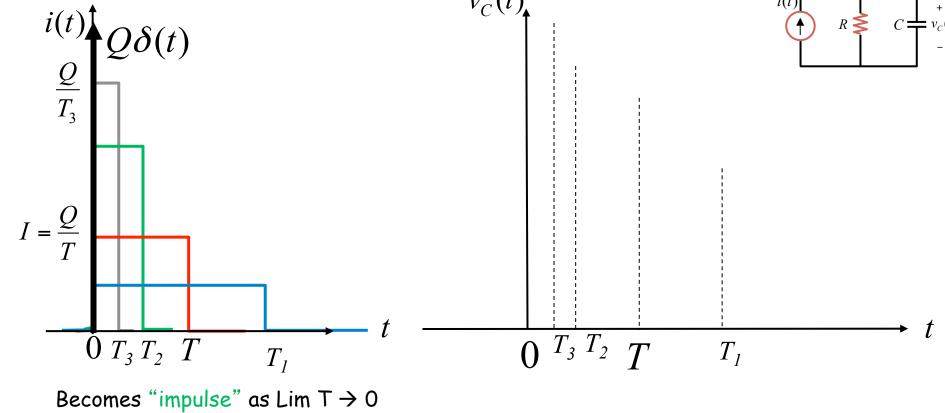
# As the pulse gets narrower $\rightarrow$ impulse





Impulse is an important signal type

Denoted by  $\delta(t)$ 

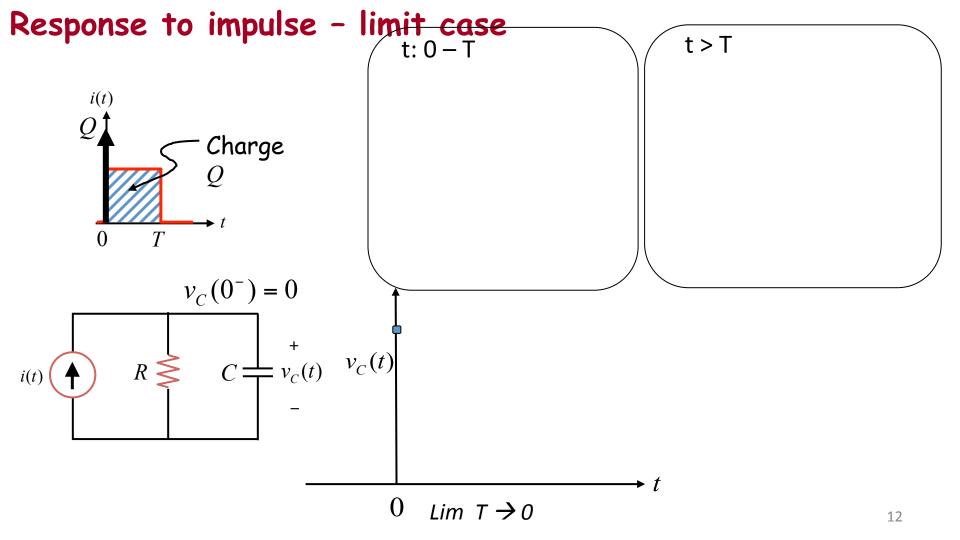


#### Response to impulse

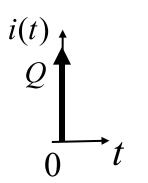

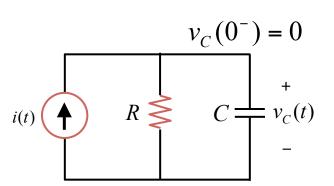




#### Current and voltage impulses

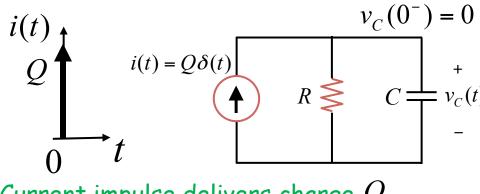



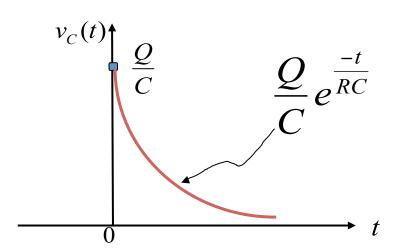


## Superposition with initial conditions and sources

### Impulses, steps and ramps

For linear systems (remember, no sources and initial conditions)

#### Back to:

## Problem:

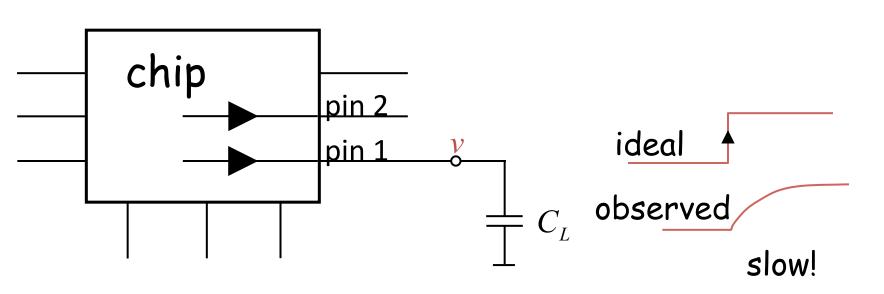


So the engineers decided to speed it up...  $\frac{R_L}{R_{ON}} \text{ made } R_L \text{ small}_{_{17}}$ 

## Slower may be better

 $\nu$ :

••• 6.002x expert saw the solution

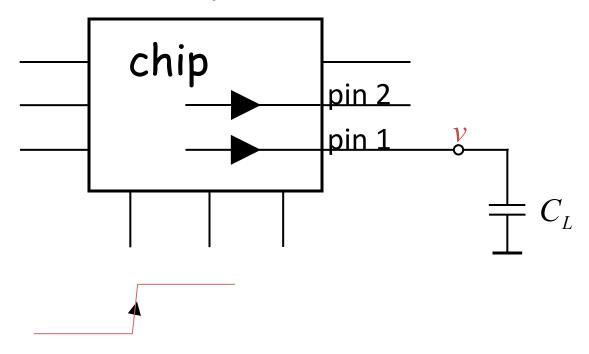


We now have the tools to understand why

Slow the edges down!

Why? Consider ...
Case 1


# Why? Consider ...

Case 2

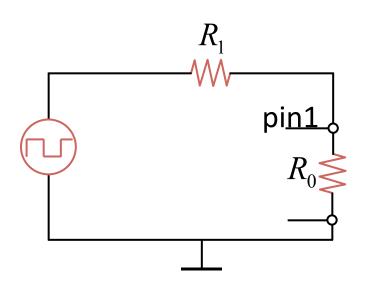


# Why? Consider ...

Model:

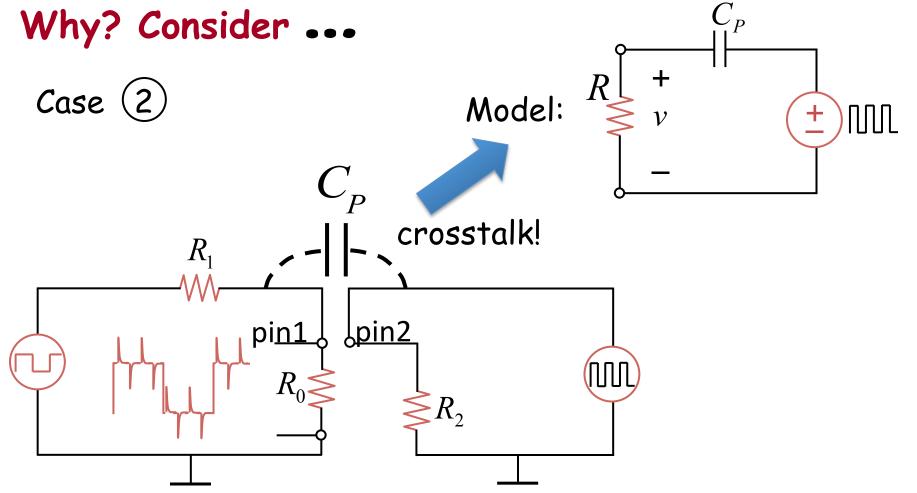

# Case 3

#### ••• 6.002x expert saw the solution

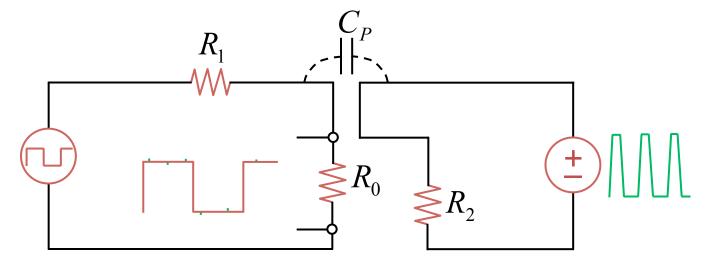

slower transitions!



## Why? Consider ...

Model:

